



SC13: Ultrasound system design: Analog front end circuits, in-probe electronics and imaging systems

3rd September 2023

www.github.com/dcowell/IUS2023-SC13

David Cowell, School of Electronic and Electrical Engineering, University of Leeds, UK

Enrico Boni, Department of Information Engineering, University of Florence, Italy

Michiel Pertijs, Electronic Instrumentation Laboratory of Delft University of Technology, Netherlands




Overview

Part 1: Ultrasound Electronics - David Cowell

- Ultrasound Instrumentation Architecture
- Basic electronics primer
- Cable Selection
- Characteristic Impedance
- Noise Factor & Noise Figure
- Impedance Matching
- Transmitter Circuitry – Analog and Switched Mode
- Transmit/Receive Switches and Multiplexers
- Receiver Analog Front End (AFE), Amplification, Filtering and Analog to Digital Convertors (ADC)


Electronics Overview

Transducer

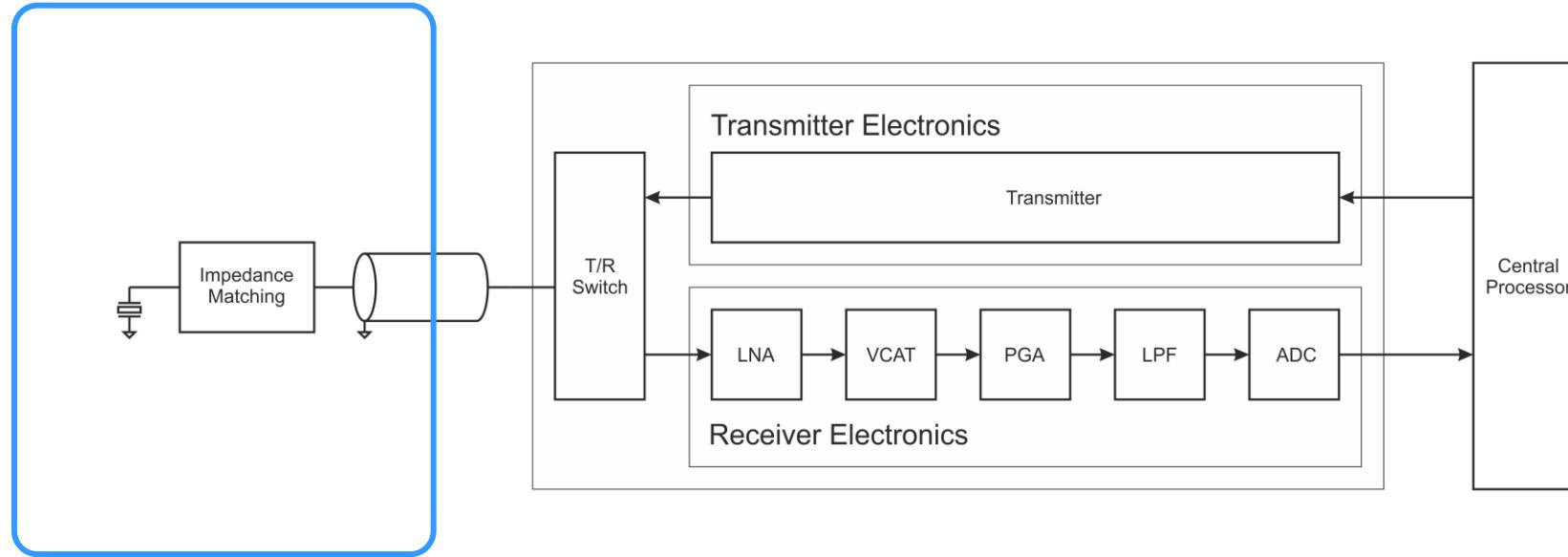


Electronics Overview

Transducer

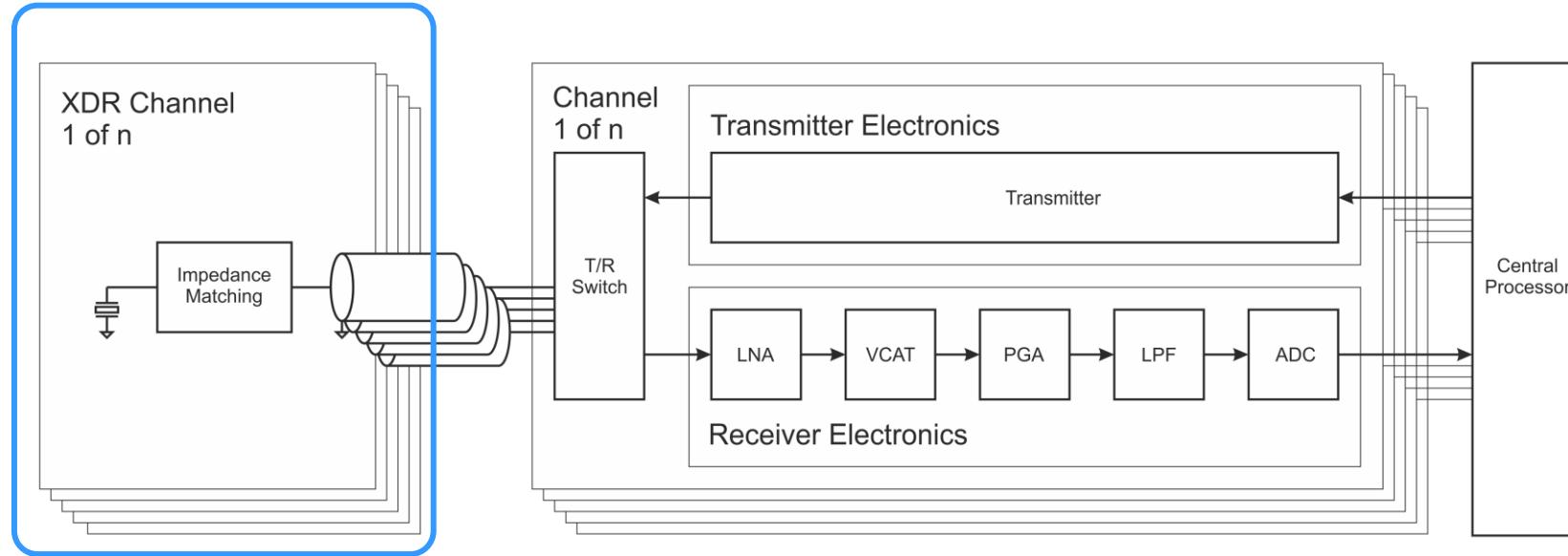

Electronics Overview

Transducer

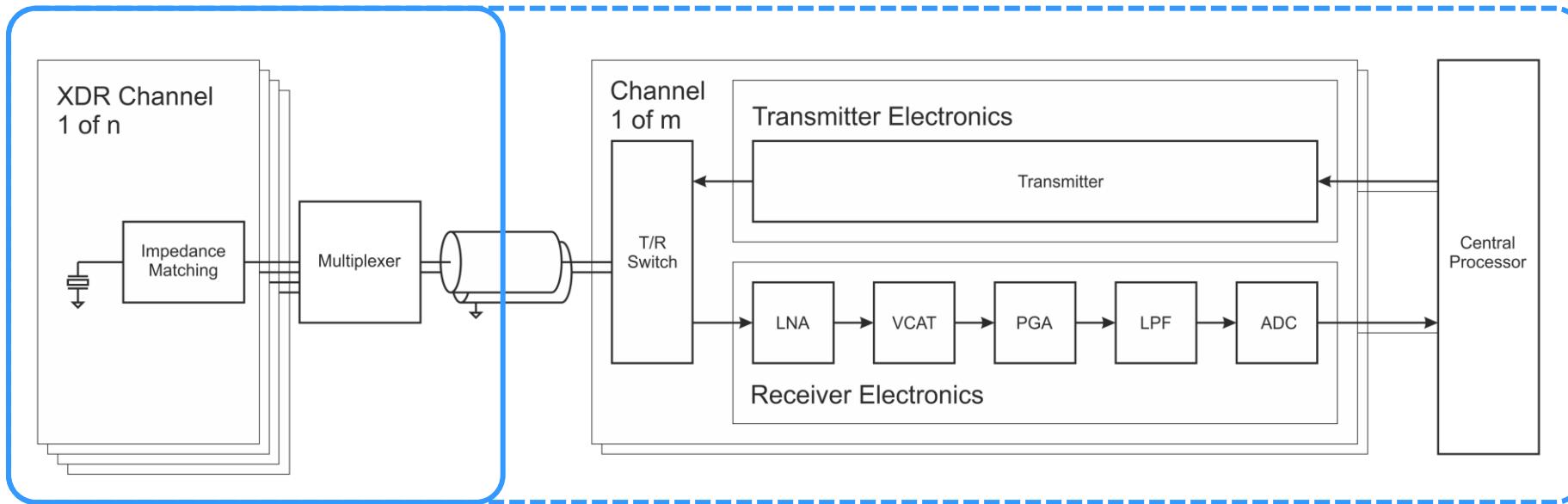

Impedance, Resistance and Reactance

Acoustic Impedance = $\frac{\text{Pressure}}{\text{Velocity}}$

$$Z = \frac{p}{v}$$

$$Z = R + jX$$


$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1} \left(\frac{X}{R} \right)$$

versus

Electrical Impedance = $\frac{\text{Voltage}}{\text{Current}}$

$$Z = \frac{V}{I}$$

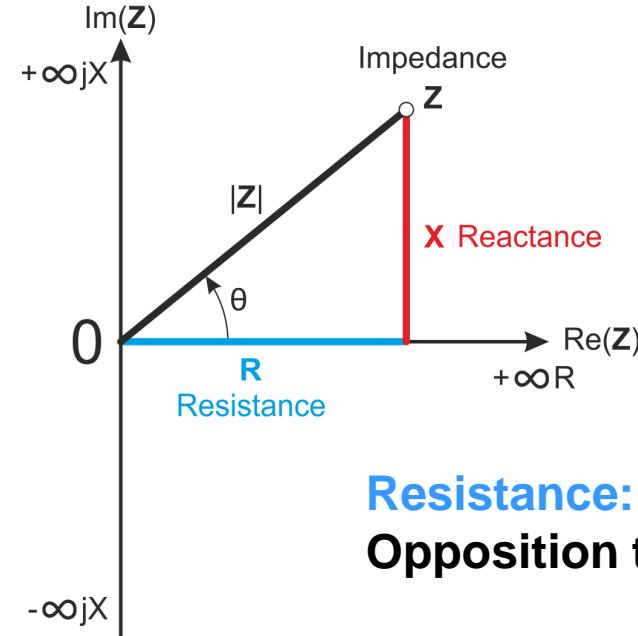

Reactance:
Opposition to the **change of electric current**

Resistance:
Opposition to the **passage of electric current**

Impedance and Admittance of Ideal Lumped Components

Impedance

Z



Resistor

$$Z = R$$



Inductor

$$Z = j\omega L$$



Capacitor

$$Z = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

Admittance

$$Y = \frac{1}{Z}$$




$$Y = \frac{1}{R}$$

$$Y = \frac{1}{j\omega L} = \frac{-j}{\omega L}$$

$$Y = j\omega C$$

Impedance of Real Lumped Components


- Real components have parasitic effects from leads or terminals and internal construction etc.
- Parasitic effects high frequencies i.e. MHz region.
- Parasitic effects can be reduced by selecting small component package size and specific high frequency components.
- Parasitic effects will alter matching circuits or filters designs from specification.
- Always simulate circuits with actual component models not ideal models.

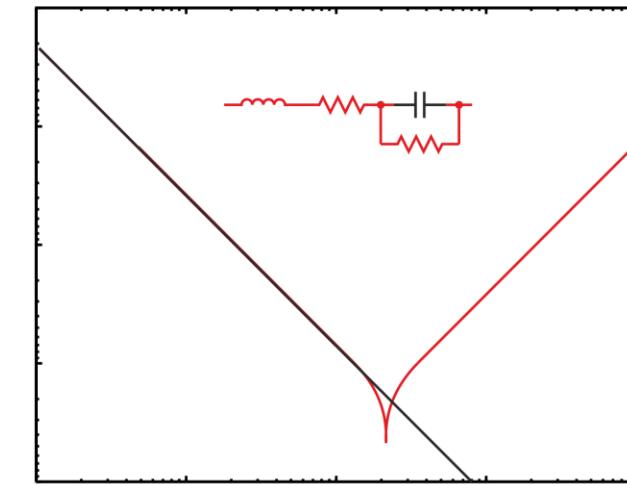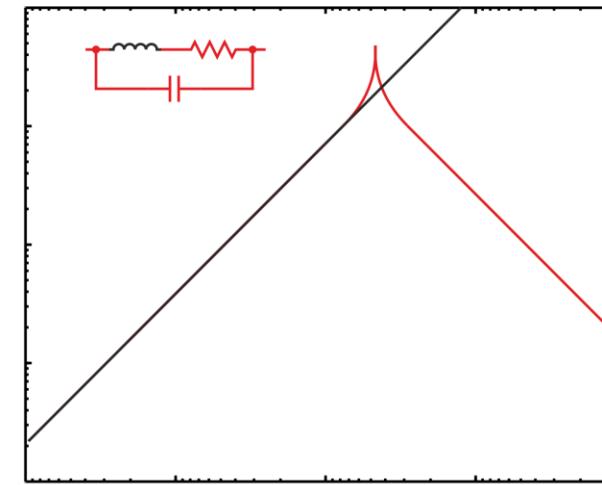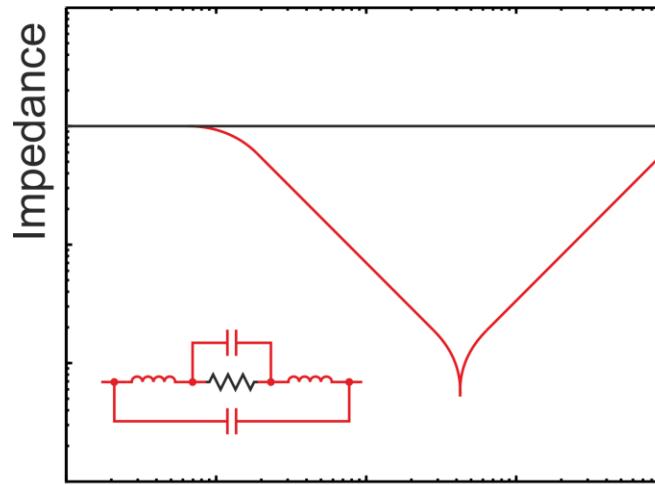

Ideal (black) and typical real response (red) for R, L, & C's.



Micro-coaxial cable

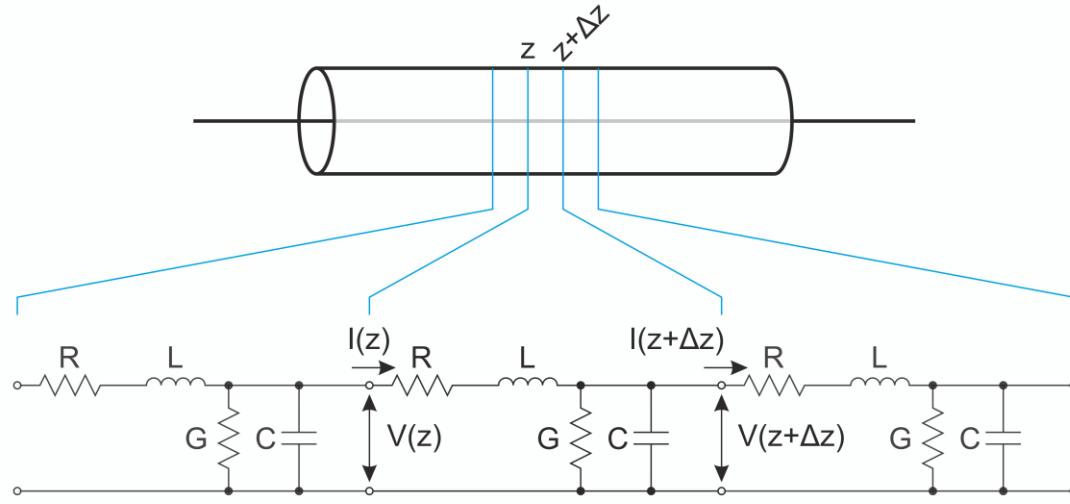

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$



- Increase characteristic impedance – decrease capacitance
 - $50\Omega - 110 \text{ pF/m}$, $60\Omega - 90 \text{ pF/m}$, $75\Omega - 60 \text{ pF/m}$, $85\Omega - 50 \text{ pF/m}$.
- Typical one way signal attenuation $\sim 0.1 \text{ dB/foot}$ ($< 10 \text{ MHz}$)
- Application will define the coaxial cable.
- Coaxial cable will define the characteristic impedance.
- Measure cable frequency dependent characteristics on a network or impedance analyser.
- Mechanical damage (twisting, kinking etc) will cause an impedance mismatch and degrade signal.



Why is Characteristic Impedance so important?

Acoustic impedance
Reflection Coefficient

$$R_p = \frac{Z_{o2} - Z_{o1}}{Z_{o2} + Z_{o1}}$$

Electrical impedance
Voltage Reflection Coefficient

$$\Gamma_{12} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

To minimize reflection and maximize transmission...
Minimize Impedance Mismatch!

Result? – Improved SNR

Noise Factor and Noise Figure

Noise Factor is noise added by a component!

$$\text{Noise Factor} = F = \frac{\text{SNR}_{\text{in}}}{\text{SNR}_{\text{out}}}$$

$$\text{Noise Figure} = \text{NF} = 10 \log F$$

$$\text{NF} = \text{SNR}_{\text{in},\text{dB}} - \text{SNR}_{\text{out},\text{dB}}$$


$$\text{NF} = (-50 - -80) - (-35 - -60)$$

$$\text{NF} = 30 - 25 = 5 \text{ dB}$$

- **Friis' Formula** $F = F_1 + \frac{F_2-1}{G_1} + \frac{F_3-1}{G_1 G_2} + \frac{F_4-1}{G_1 G_2 G_3} + \dots + \frac{F_n-1}{G_1 G_2 G_3 \dots G_{n-1}}$


where F is noise factor and G is power gain (both linear units)

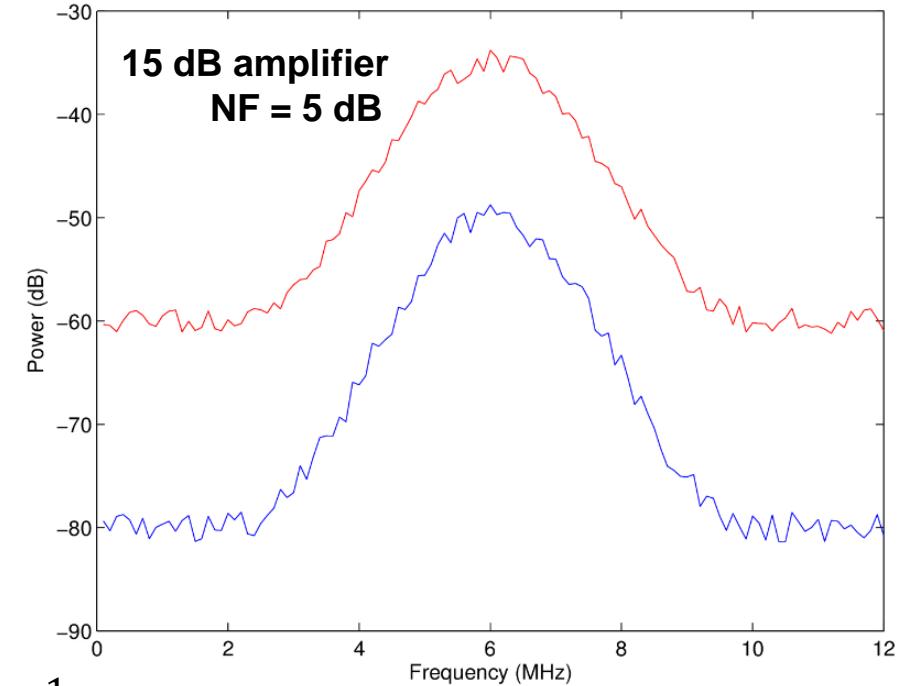- The first component, F_1 , has the most significant effect in a chain.
- Effort should be paid to improving input SNR and reducing the Noise Figure of the first component, then subsequent components in the signal chain.




Impedance Matching

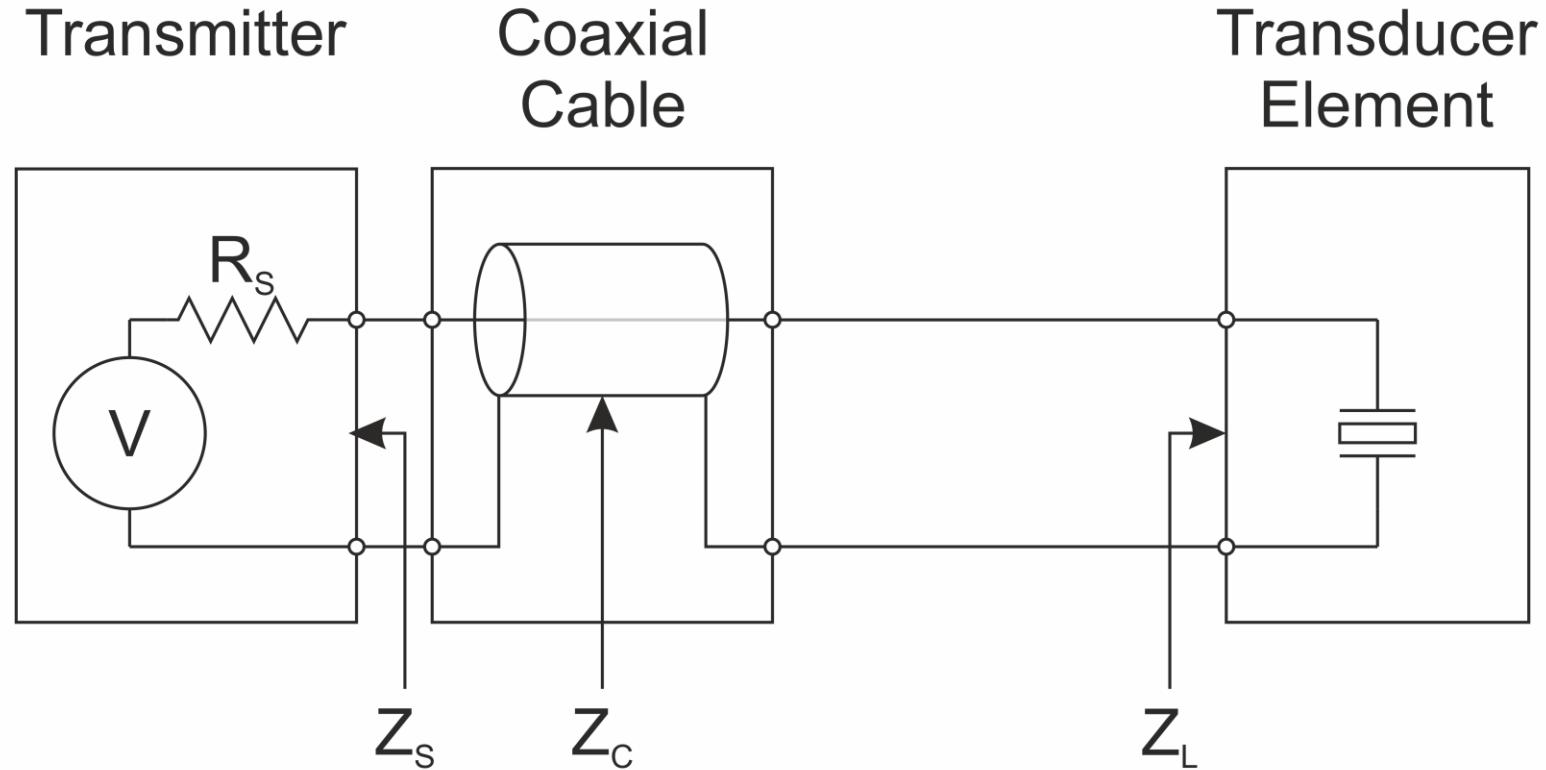- Z_s and Z_c equal to Characteristic Impedance
- Z_L not equal to Characteristic Impedance




Impedance Matching

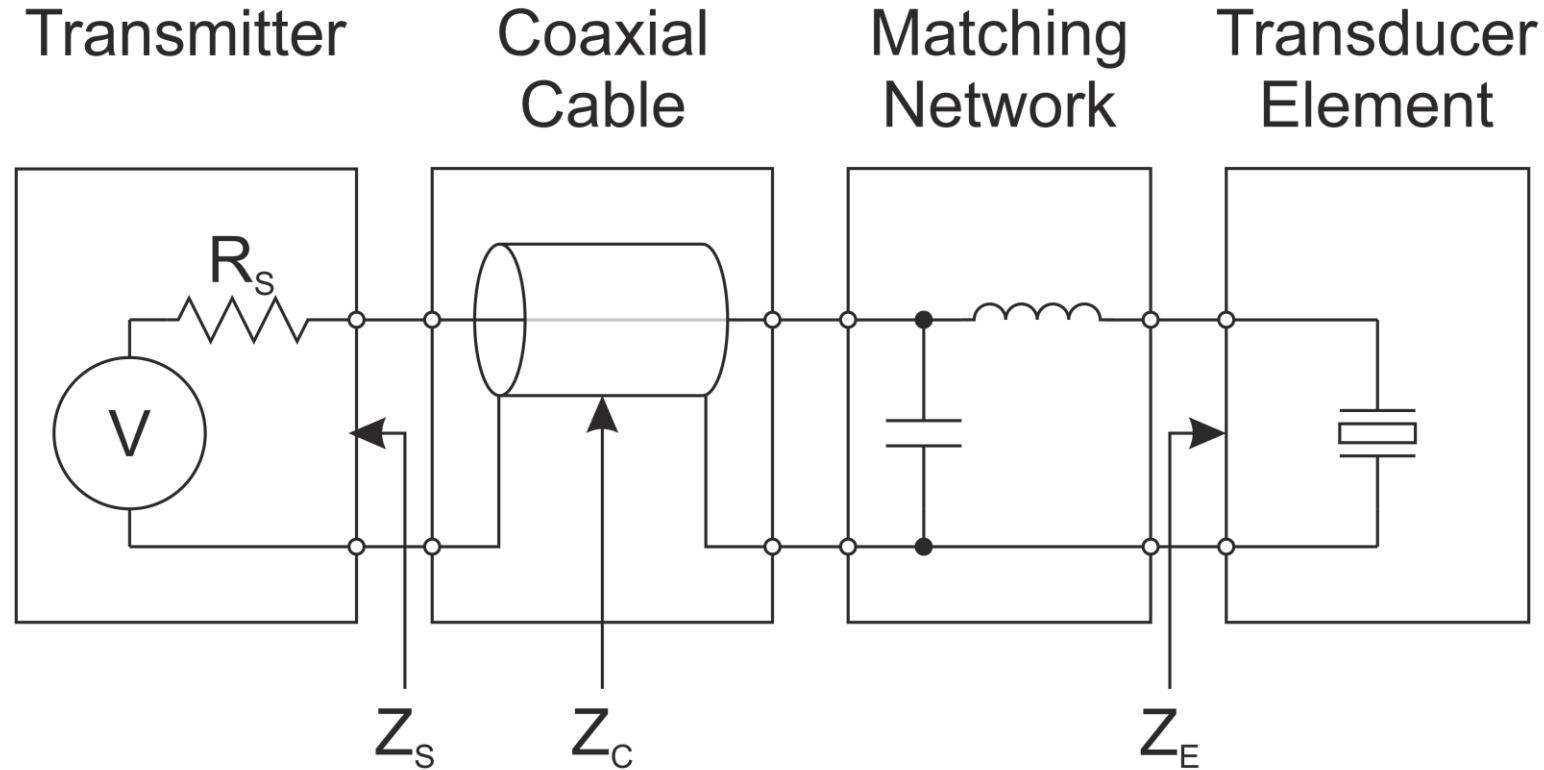- Adding a Matching Network of passive components between the coaxial cable and the transducer element allows impedance transformation




Impedance Matching

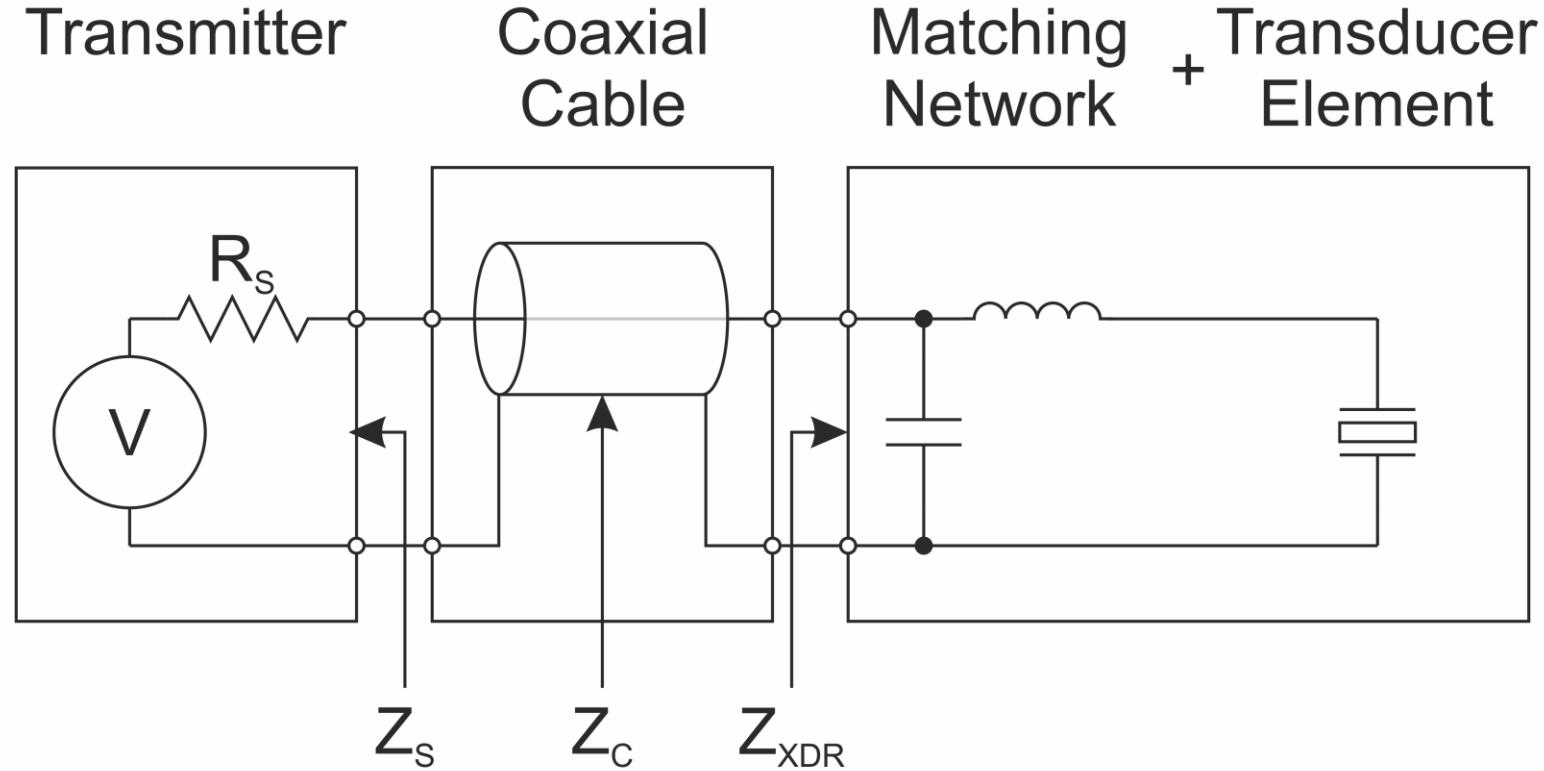- When $Z_s = Z_c = Z_{XDR}$
 - Maximum transmission of energy from transmitter to transducer



Impedance Matching

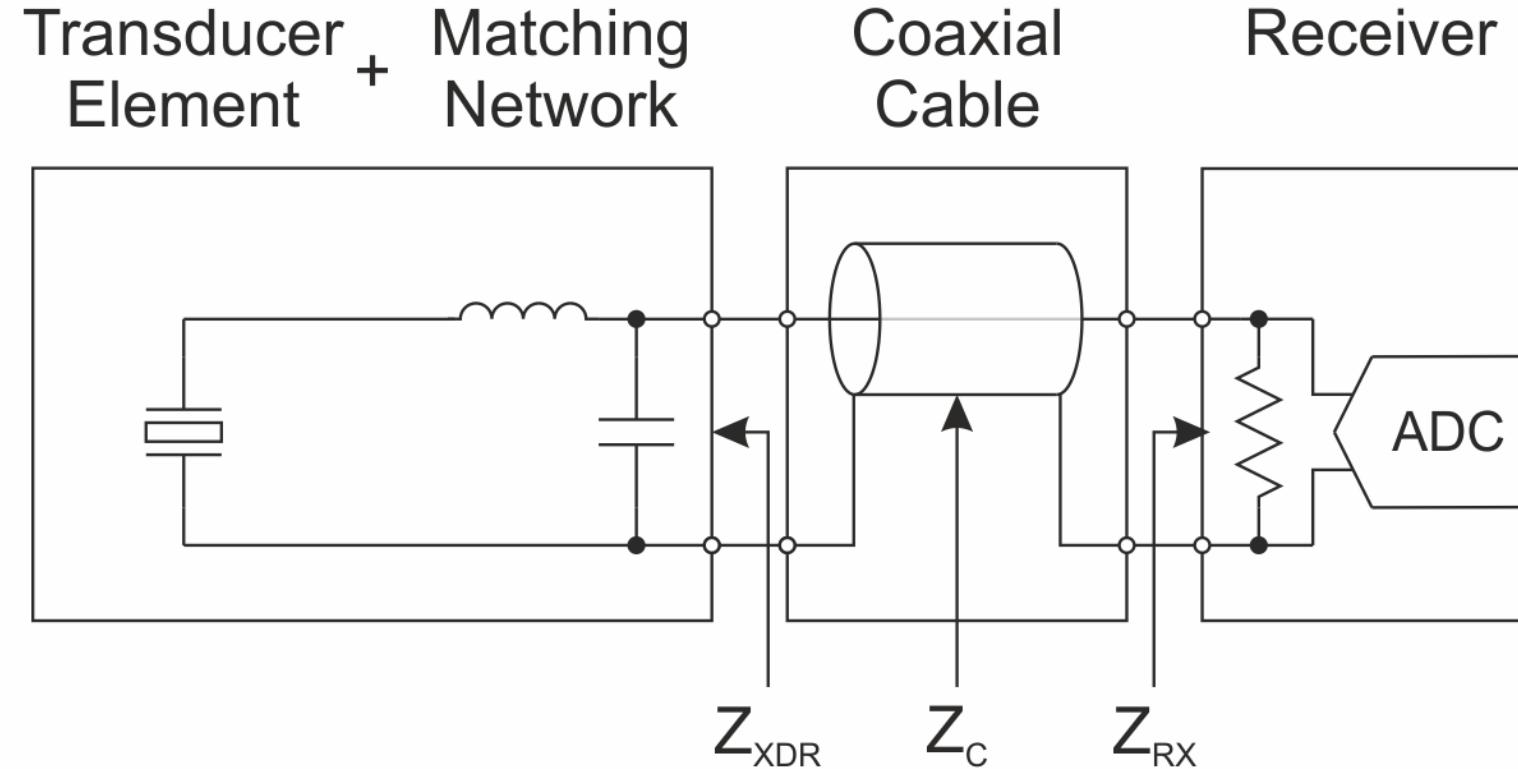
- When $Z_{XDR} = Z_C = Z_{RX}$
 - Maximum transmission of energy from transducer to receiver



Single component Impedance Matching

Aim

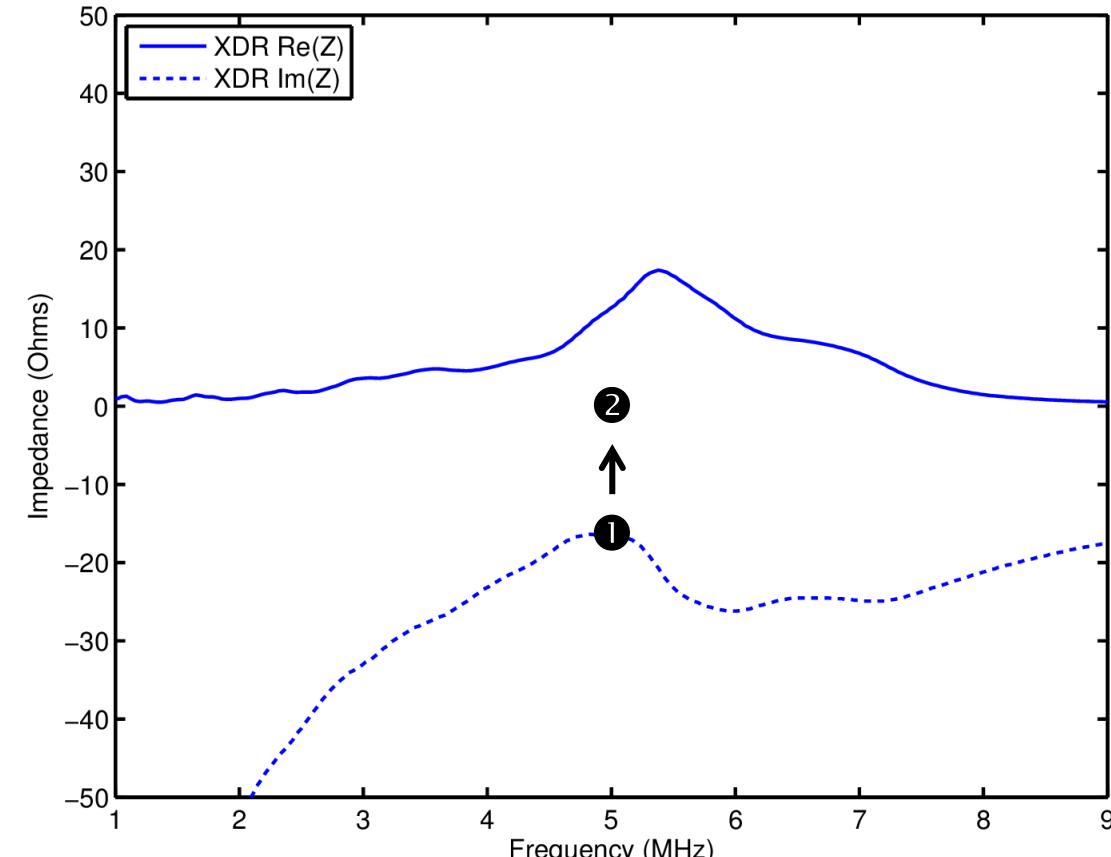With a single component reduce reactance to zero at 5 MHz
Calculate required change in reactance from ① to ② -j16.6 Ω to j0Ω




Single component Impedance Matching


- Calculate required component to add $j16.6 \Omega$ at 5MHz

$$L_S = \frac{Z}{j\omega} = \frac{16.6j}{j2\times\pi\times5\times10^6} = 0.528 \mu\text{H}$$


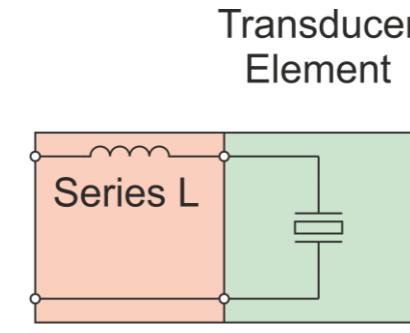
- Add series inductor to complex impedance of transducer element.



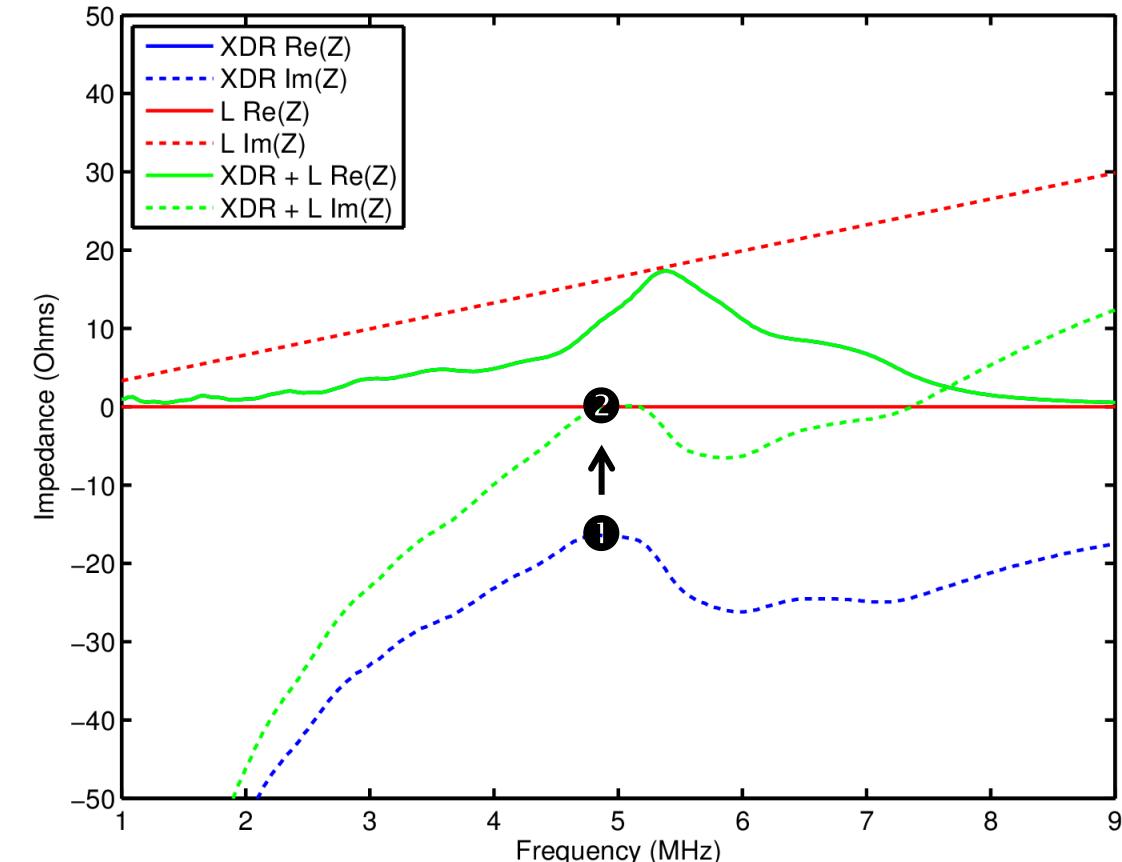- Reactance cancelled at 5 MHz with no change in resistance.
- However, impedance changed from 20.8 ohms to 12.5 ohms!




Impedance Visualisation Smith Charts

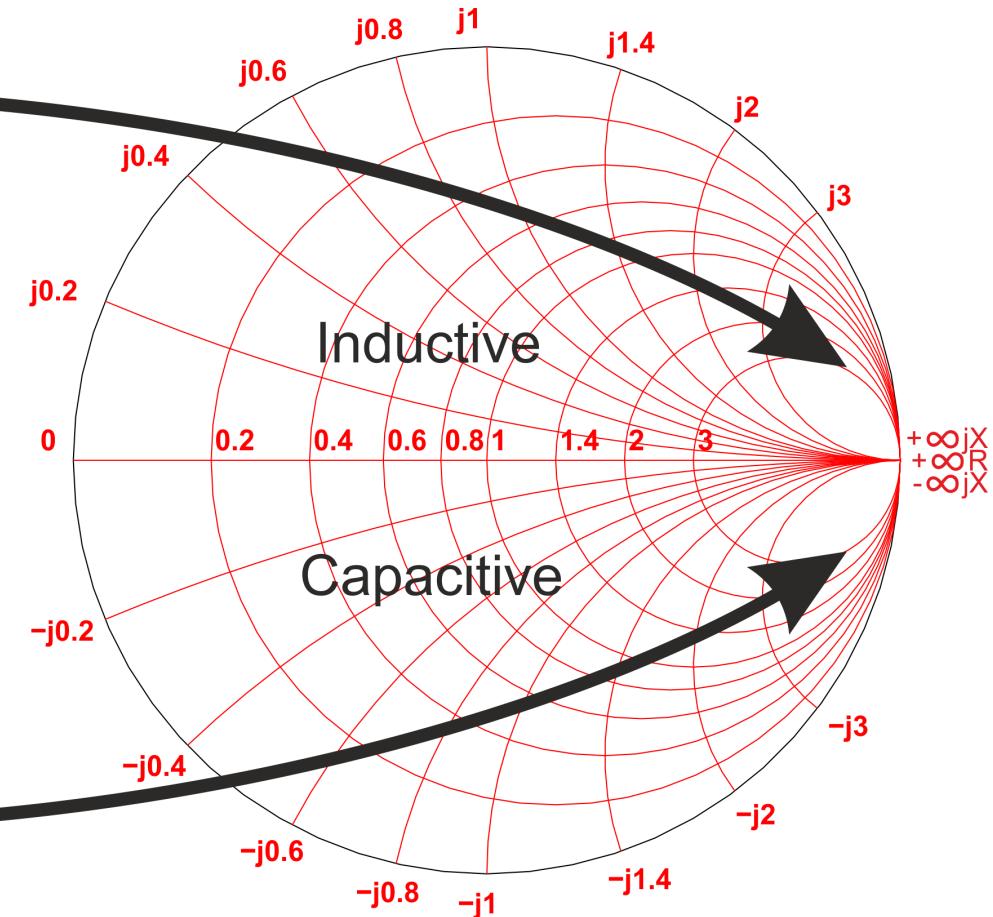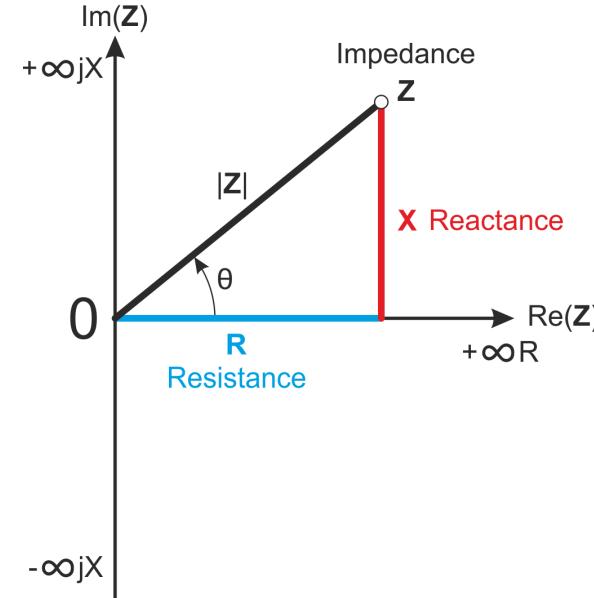

Smith Chart - Impedance

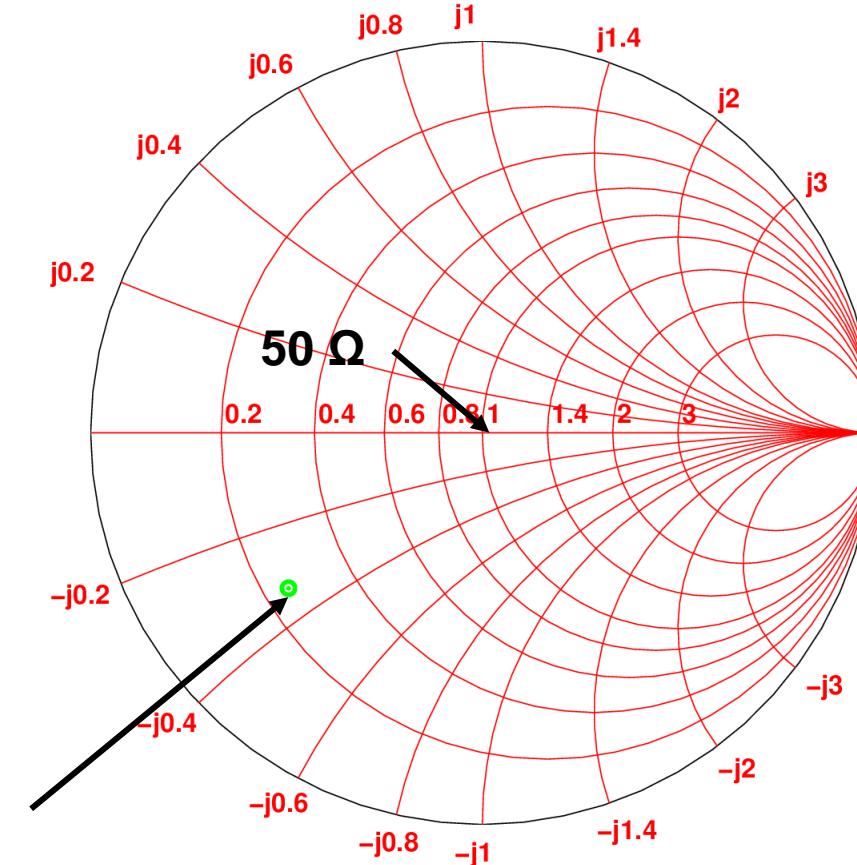
- Graphical tool for displaying and manipulating impedances.
 - Extensively used in Electronic Engineering for calculating impedance matching circuits.
 - Often found on impedance or network analyser instruments.
 - Typically matched to characteristic (system) impedance.
- $Z_n = Z/Z_o$ e.g. ($Z_o = 50$)
- Example XDR at 5 MHz
- $$Z_n = \frac{12.5 - j16.6\Omega}{50} = 0.25 - j0.33 \Omega$$





Smith Chart - Admittance

- Graphical tool for displaying and manipulating admittances.
- Rotation of the smith chart by 180 degrees.
- Typically matched to characteristic (system) impedance.
- $Y_o = \frac{1}{Z_o}$ e.g. $Y_o = \frac{1}{50} = 0.02$
- $Y_n = \frac{Y}{Y_o} = Y \times Z_o$
- Example XDR at 5 MHz
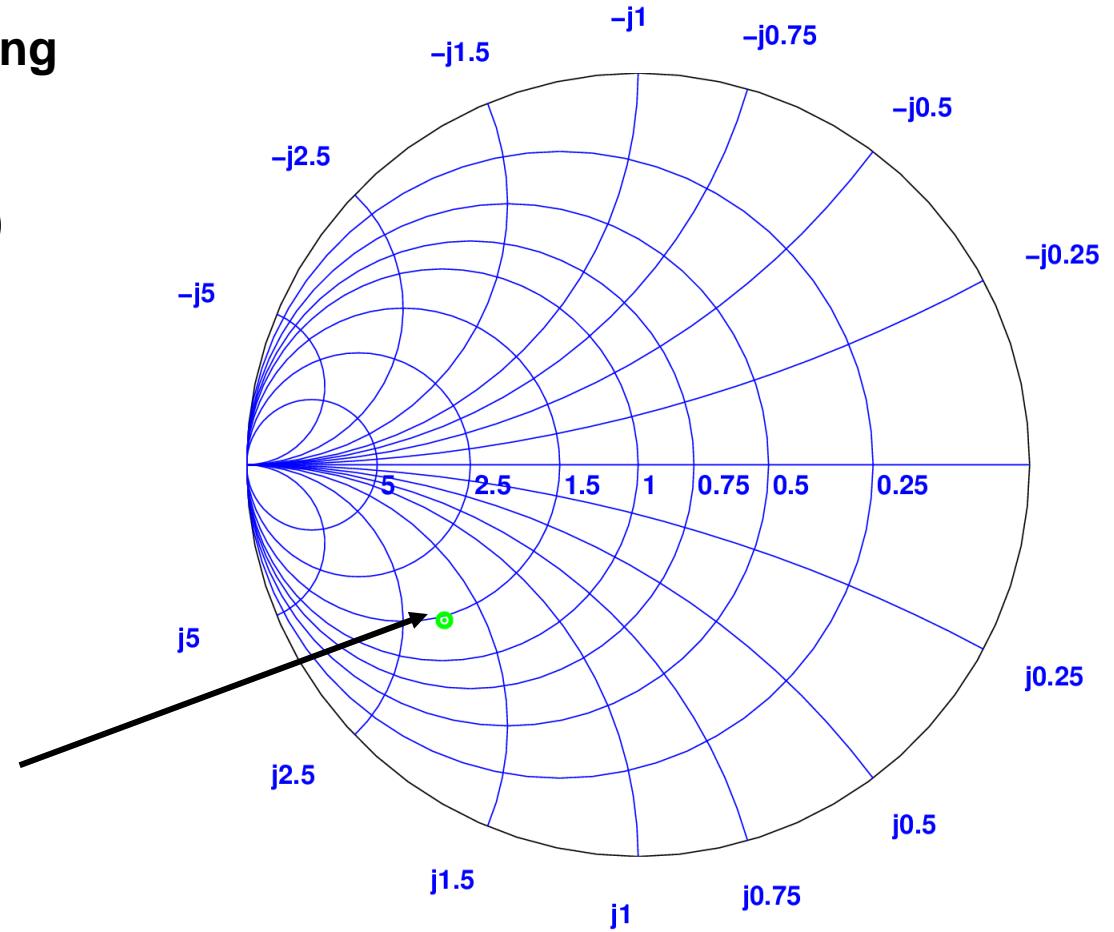
$$Y_n = \frac{50}{12.5 - j16.6} = 1.45 + j1.9 \text{ S}$$





Smith Chart – Impedance-Admittance

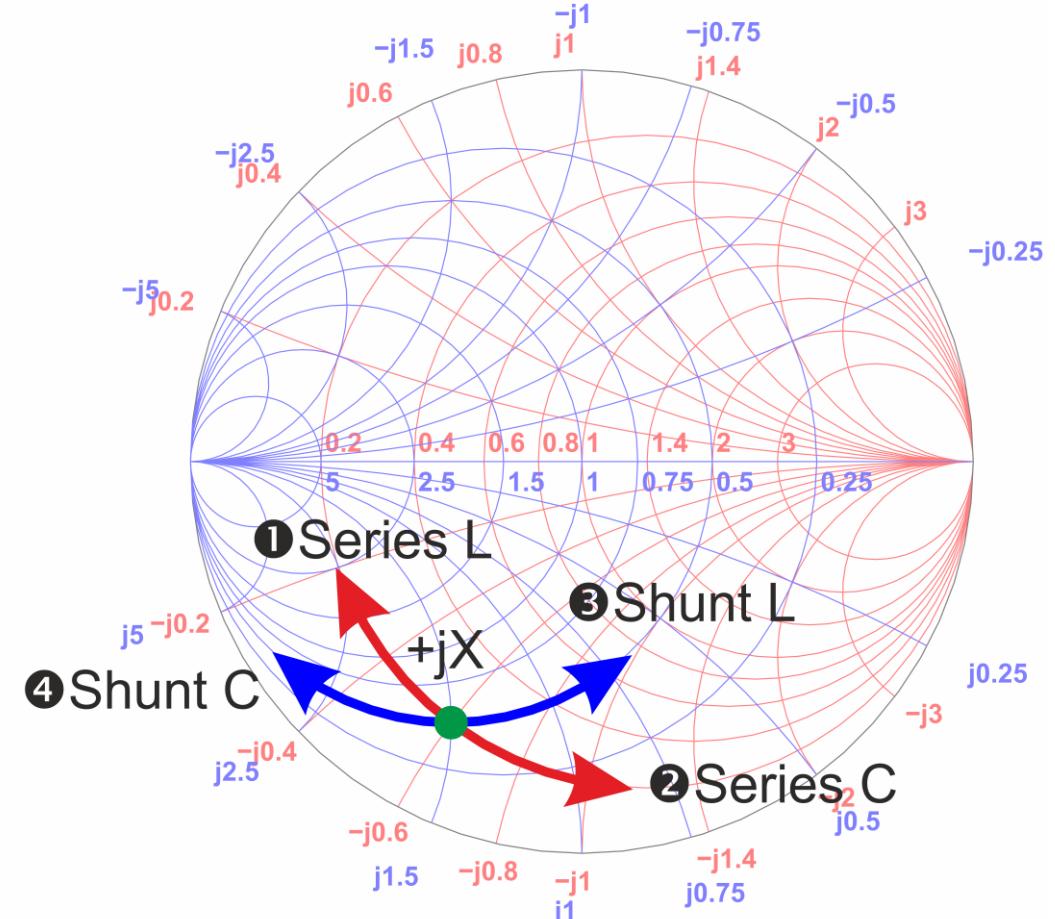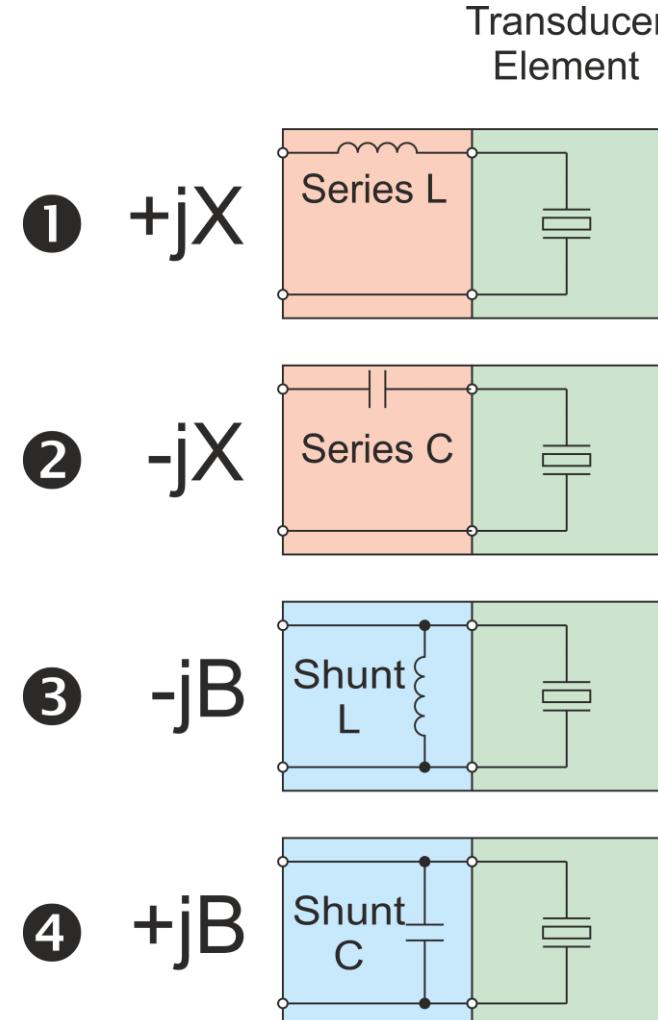

Smith Chart Impedance Matching

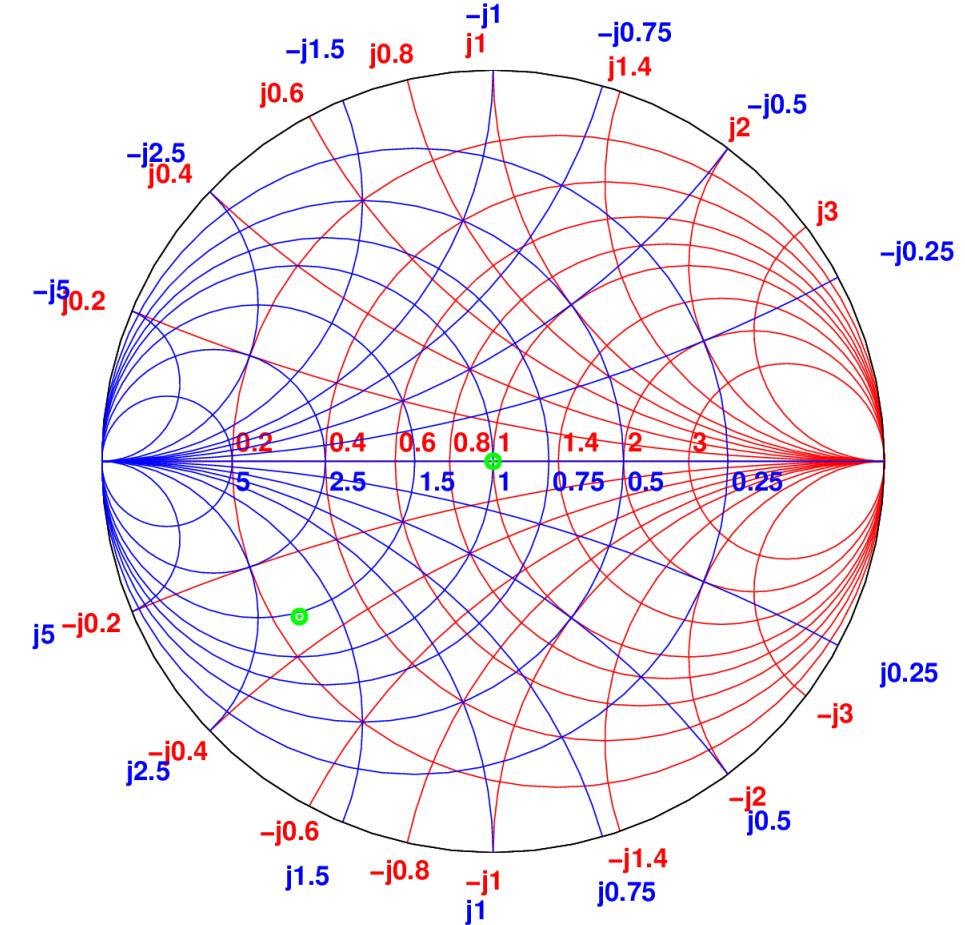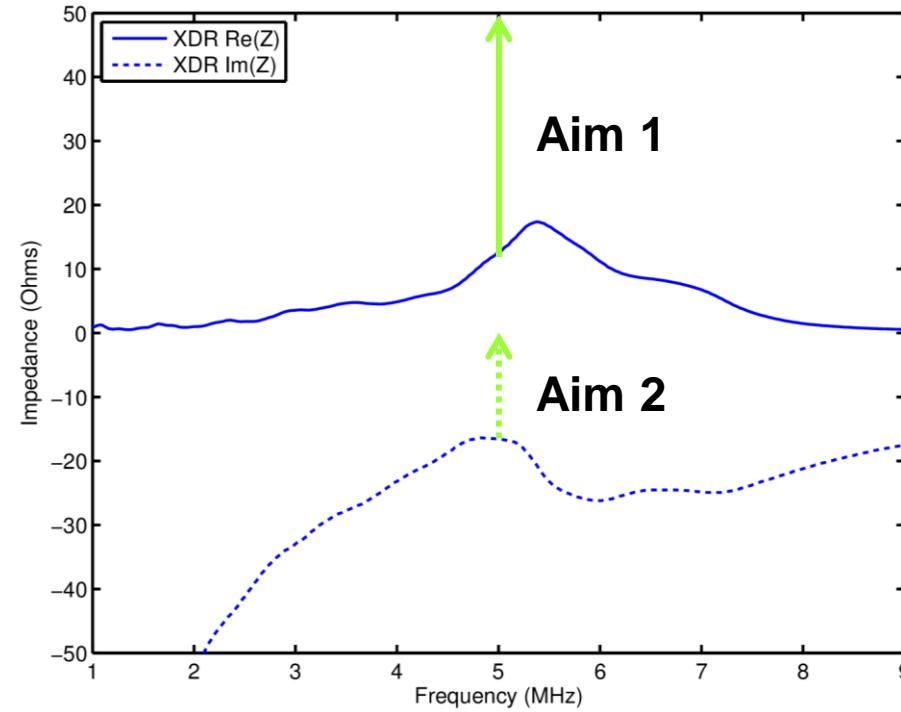Aim 1 Resistance of 50 ohms at 5 MHz
Aim 2 Reactance of 0 ohms at 5 MHz



Smith Chart Impedance Matching Series Inductor

Unmatched transducer impedance shown in BLACK


At nominal frequency of 5 MHz: $Z_{XDR} = 12.5 - j16.6\Omega$

$$\textcircled{1} \text{ On smith chart: } Z_n = \frac{12.5 - j16.6\Omega}{50} = 0.25 - j0.33\Omega$$

Therefore, add $j16.6\Omega$ at 5 MHz
to cancel capacitive impedance.

$$L_S = \frac{Z}{j\omega} = \frac{16.6j}{j2\pi\times5\times10^6} = 0.528 \mu\text{H}$$

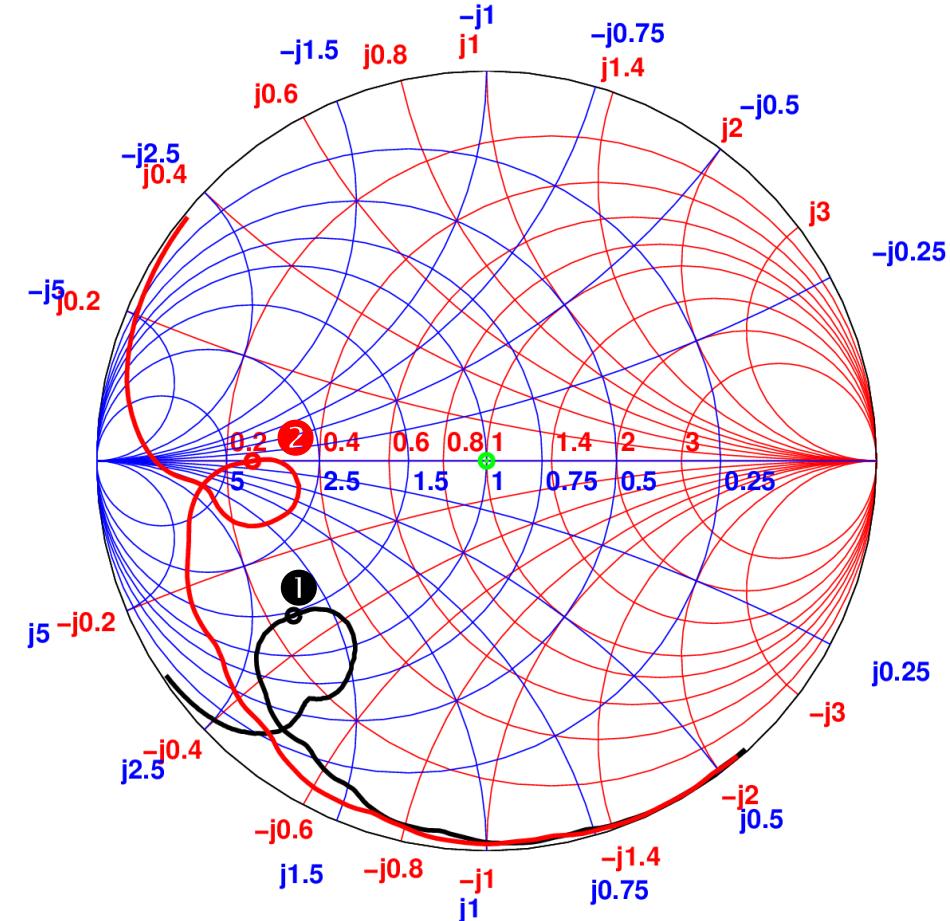Adding a series inductor of value of $0.528 \mu\text{H}$
rotates **①** anticlockwise around Inductance Smith Chart
to 12.5Ω (zero phase) **②**.



Smith Chart Impedance Matching Shunt Inductor

Unmatched transducer impedance shown in BLACK

At nominal frequency of 5 MHz:

Convert impedance to admittance:

$$Y_{XDR} = \frac{1}{12.5 - j16.6} = 0.029 + j0.038 \text{ S}$$


① On smith chart: $Y_n = 50 \times Y_{XDR} = 1.45 + j1.9 \text{ S}$

Therefore, subtract $j0.038 \text{ S}$ at 5 MHz
to cancel capacitive impedance.


$$L_P = \frac{1}{j\omega Y} = \frac{1}{j2 \times \pi \times 5 \times 10^6 \times j0.038} = 0.837 \mu\text{H}$$

Adding a shunt (parallel) inductor of value $0.837 \mu\text{H}$
rotates ① anticlockwise around Admittance Smith Chart
to 34.5Ω (0.029 S) ③.

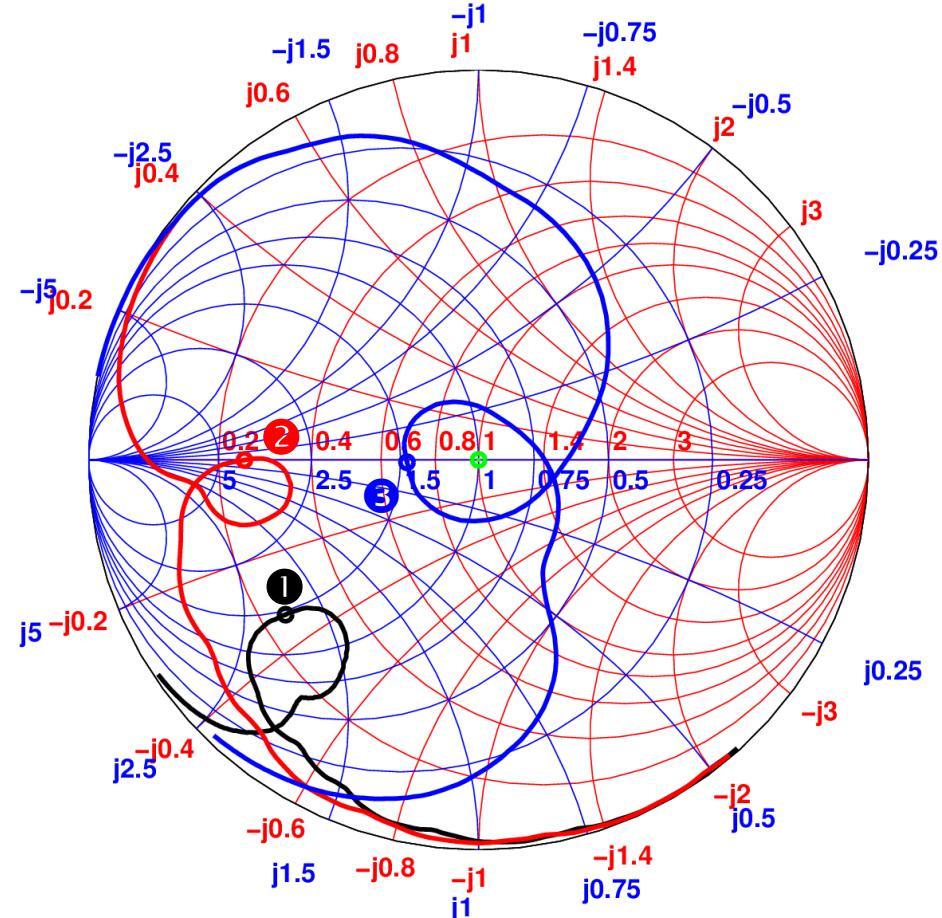
Note: Impedance circles 50Ω indicating good matching over a broad bandwidth.



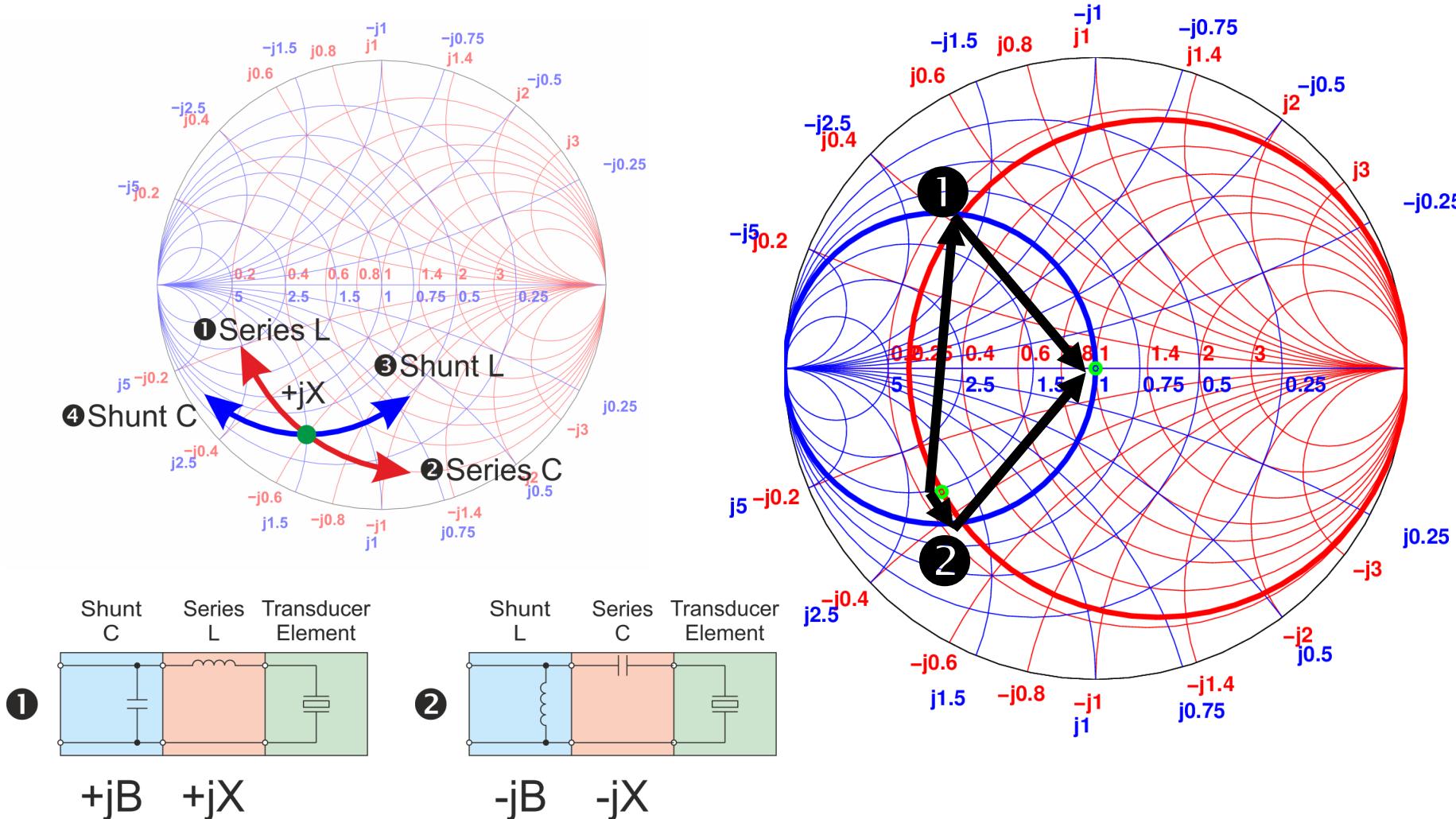Multi-component Smith Chart Impedance Matching



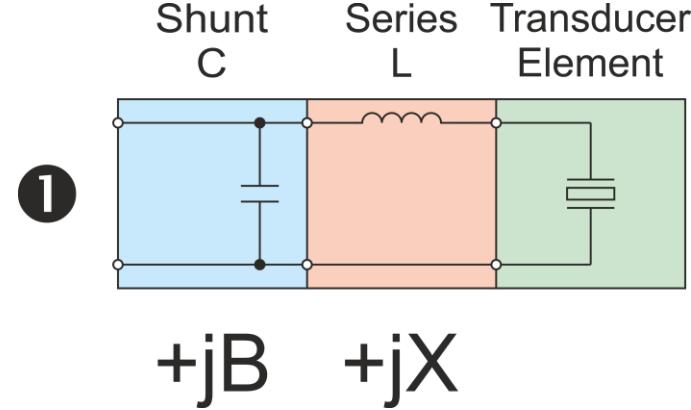1 Multi-component Smith Chart Impedance Matching




S: $Z_{XDR} = 12.5 - j16.6$

S: $Z_{XDRn} = 0.25 - j0.33$

M: $Z_{(XDR+L)n} = 0.25 + j0.43$

M-S: $Z_{Ln} = 0 + j0.76 \therefore Z_L = j38$

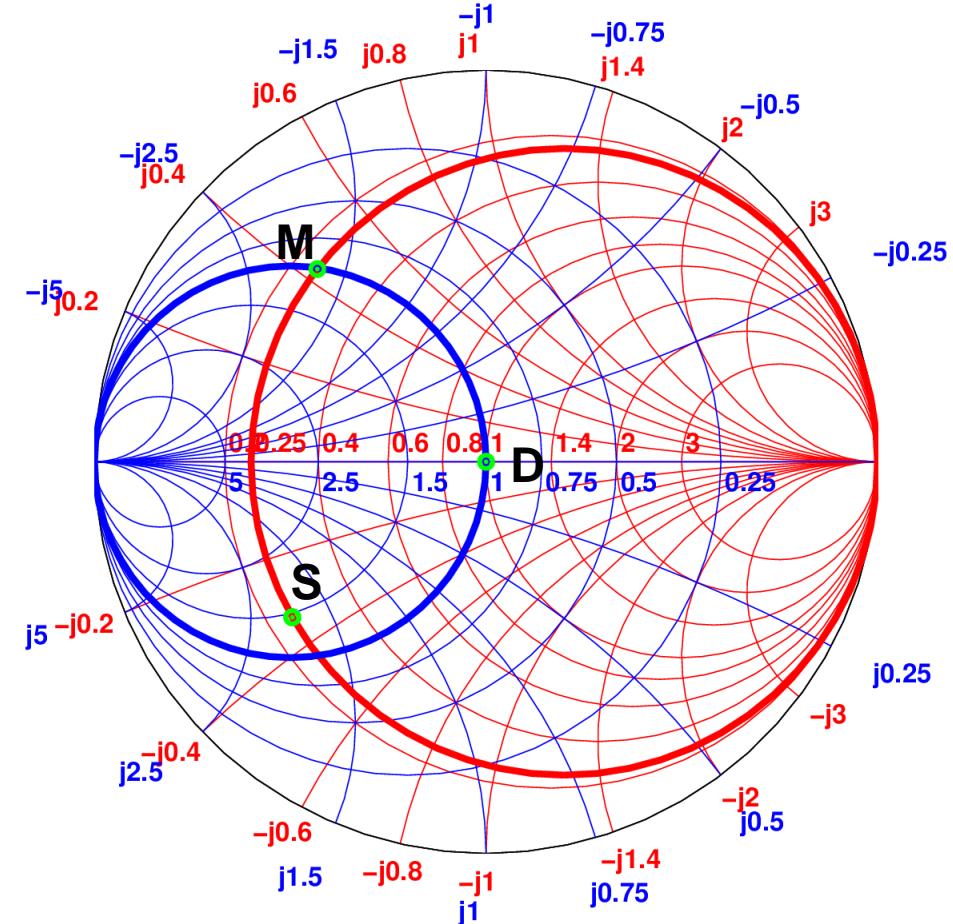
At 5 MHz $L = \frac{j38}{j2\pi \times 5e6} = 1.2\mu H$





I Multi-component Smith Chart Impedance Matching

UNIVERSITY OF LEEDS

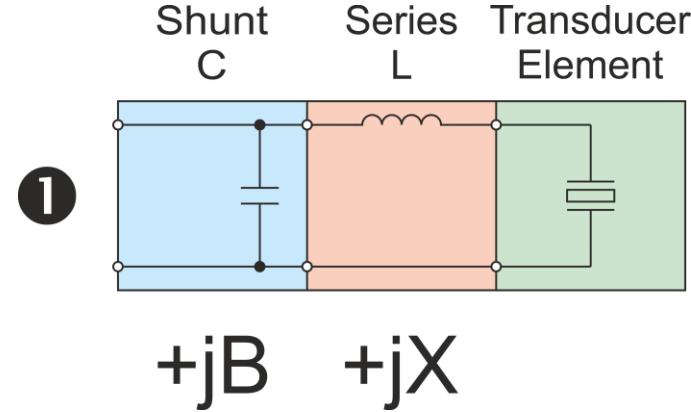


M: $Z_{(XDR+L)n} = 0.25 + j0.43$

M: $Y_{(XDR+L)n} = 1 - j1.74$

D: $Y_{(XDR+L)n||Cn} = 1 - j0$


D-M: $Y_{Cn} = 0 + j1.74 \quad \therefore \quad Y_C = j0.348$

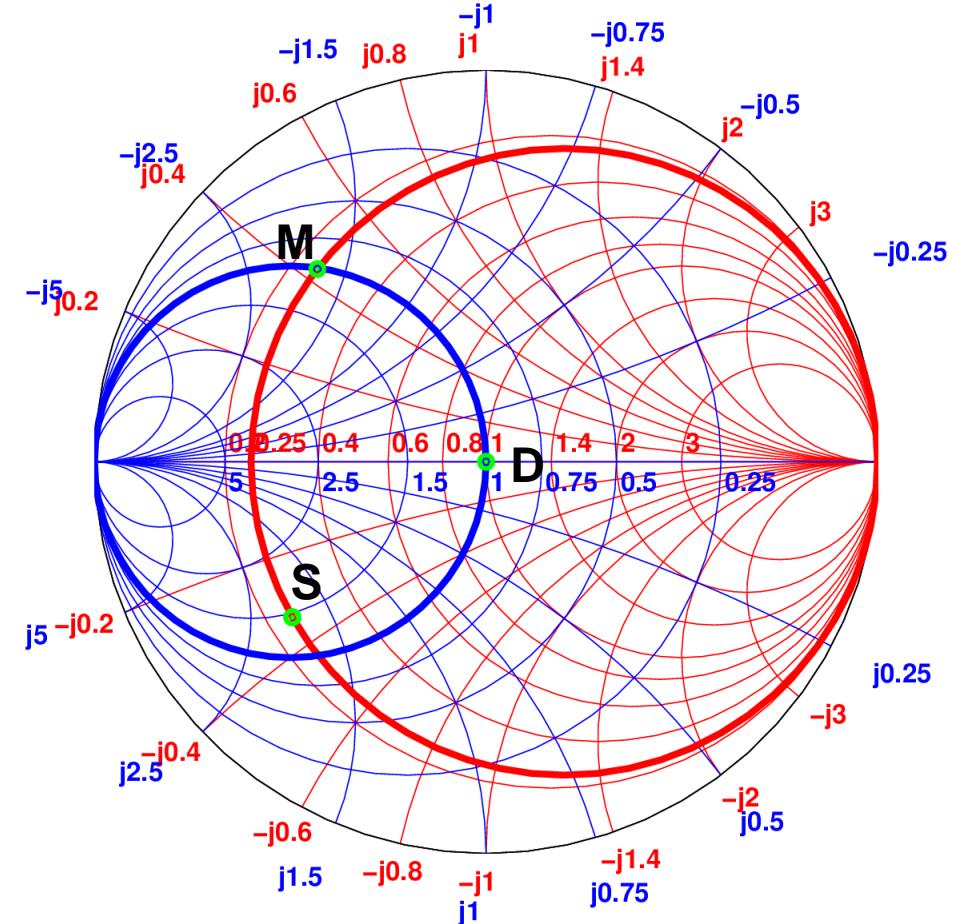At 5 MHz $C = \frac{j0.348}{j2\pi \times 5e6} = 1.1nF$



②

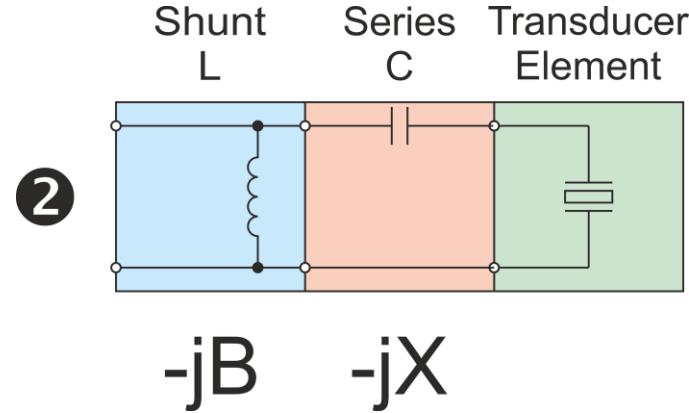Multi-component Smith Chart Impedance Matching




S: $Z_{XDR} = 12.5 - j16.6$

S: $Z_{XDRn} = 0.25 - j0.33$

M: $Z_{(XDR+C)n} = 0.25 - j0.43$


M-S: $Z_{Cn} = 0 - j0.10 \therefore Z_C = -j5$

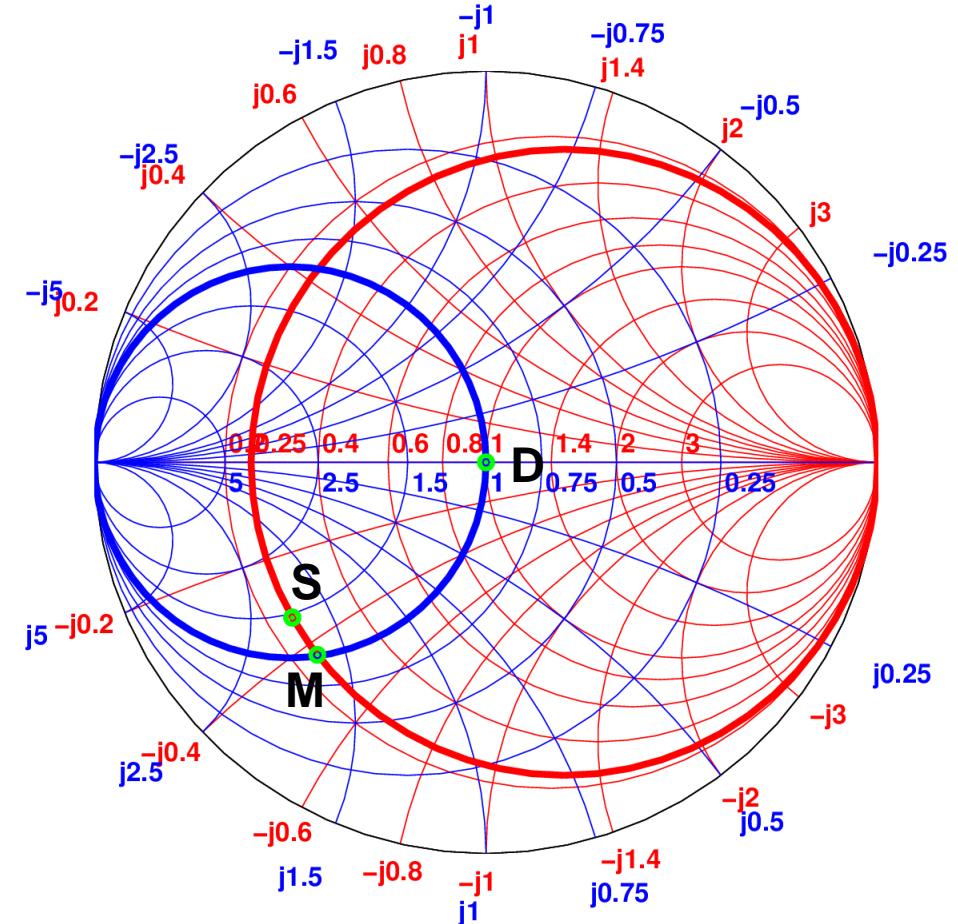At 5 MHz $C = \frac{1}{j2\pi \times 5e6 \times (-j5)} = 6.36nF$



②

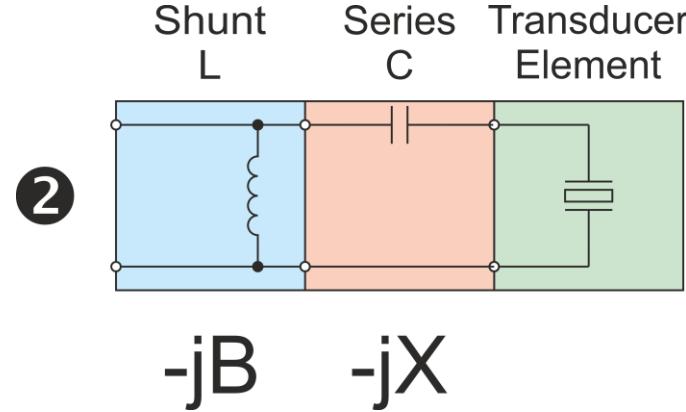Multi-component Smith Chart Impedance Matching




$$\mathbf{M: } Z_{(XDR+C)n} = 0.25 - j0.43$$

$$\mathbf{M: } Y_{(XDR+C)n} = 1 + j1.73$$



$$\mathbf{D: } Y_{(XDR+C)n||Ln} = 1 + j0$$

$$\mathbf{D-M: } Y_{Ln} = 0 - j1.73 \quad \therefore \quad Y_L = -j0.035$$


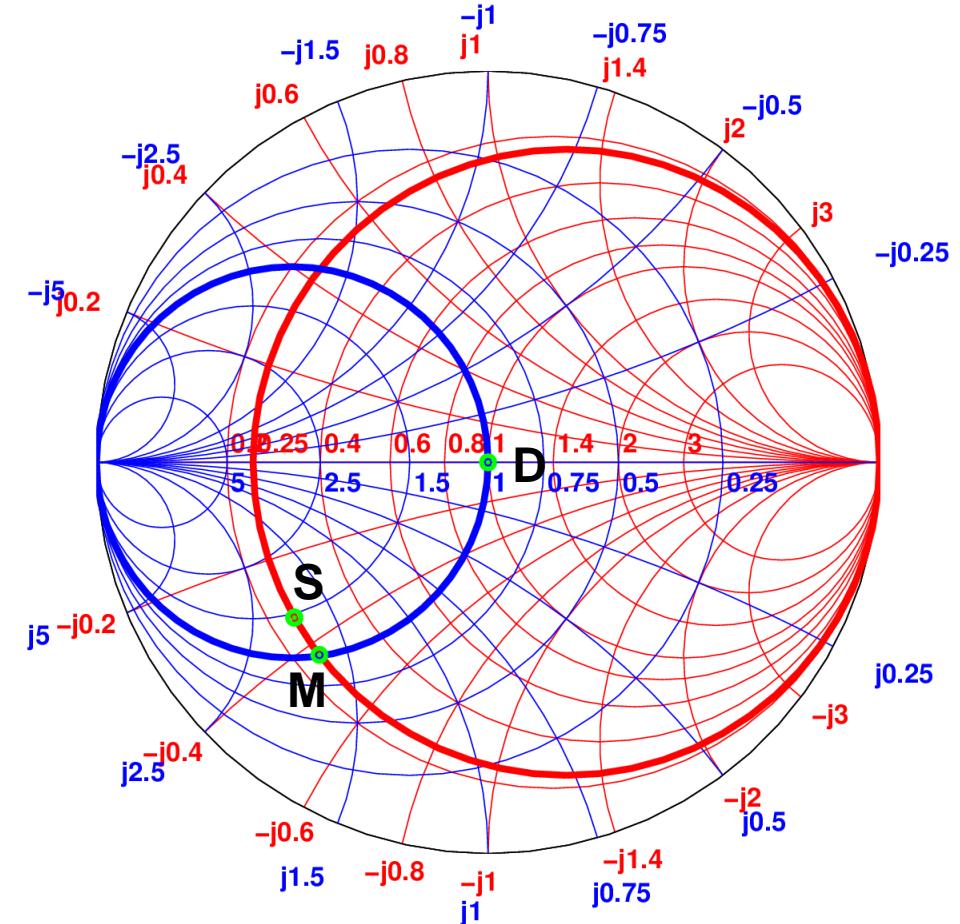
$$\text{At 5 MHz} \quad L = \frac{1}{j\omega Y} = \frac{1}{j2\pi \times 5e6 \times (-j0.035)} = 917nH$$



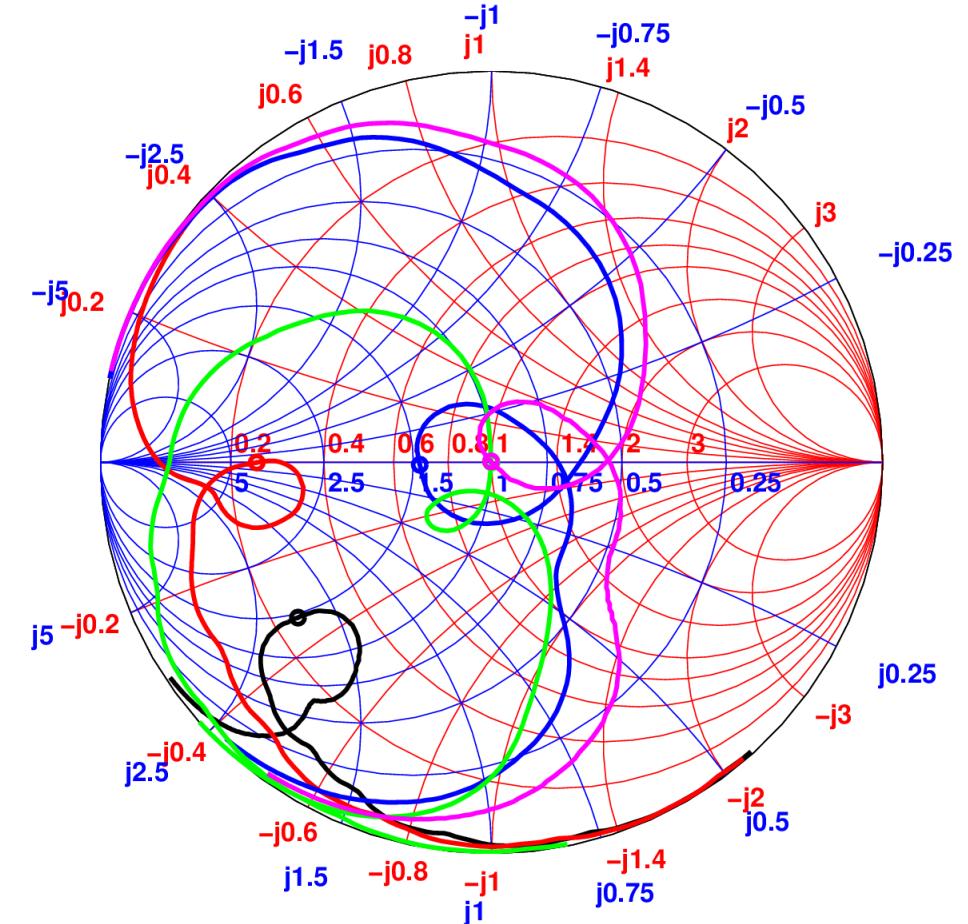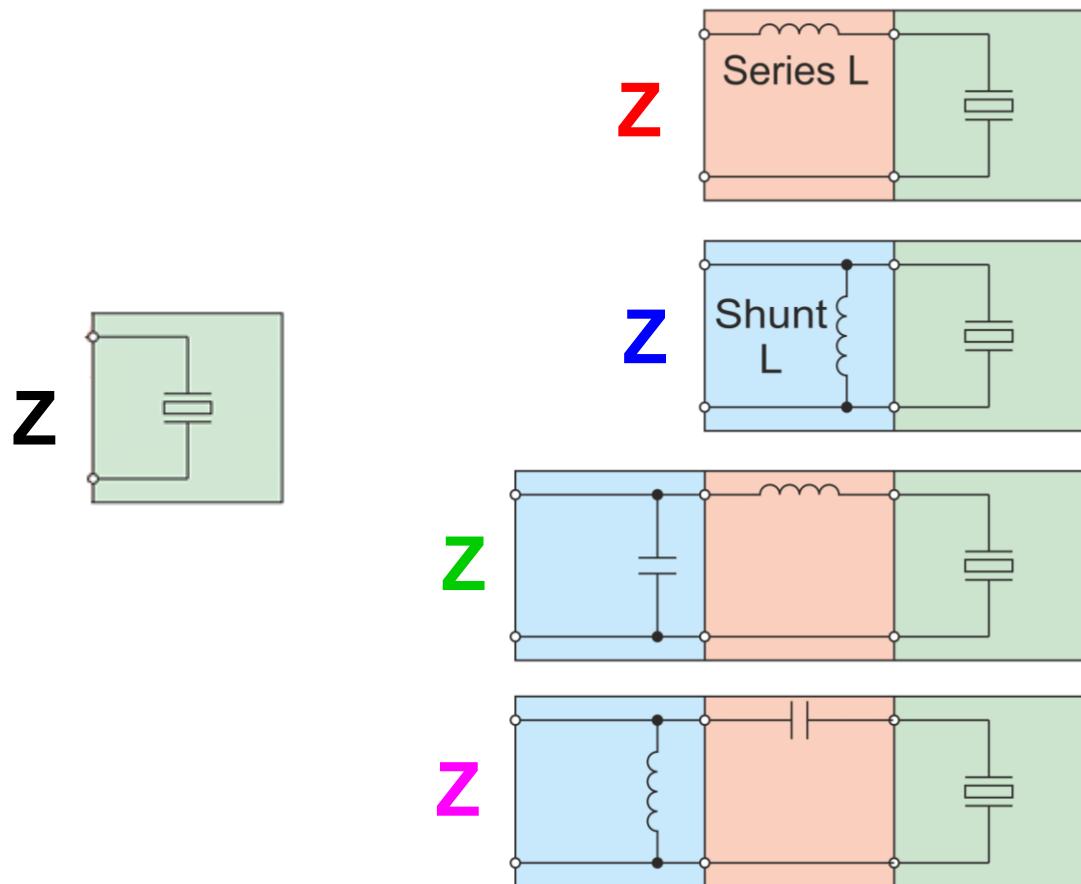
Multi-component Smith Chart Impedance Matching



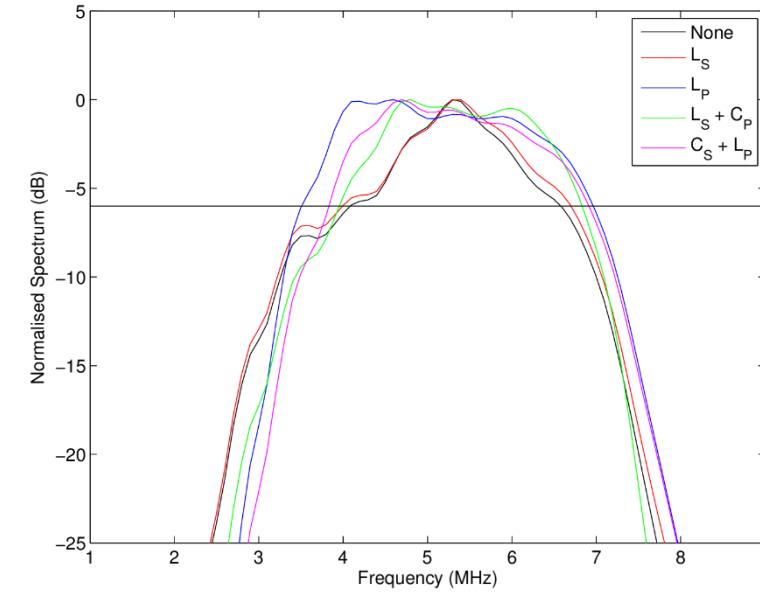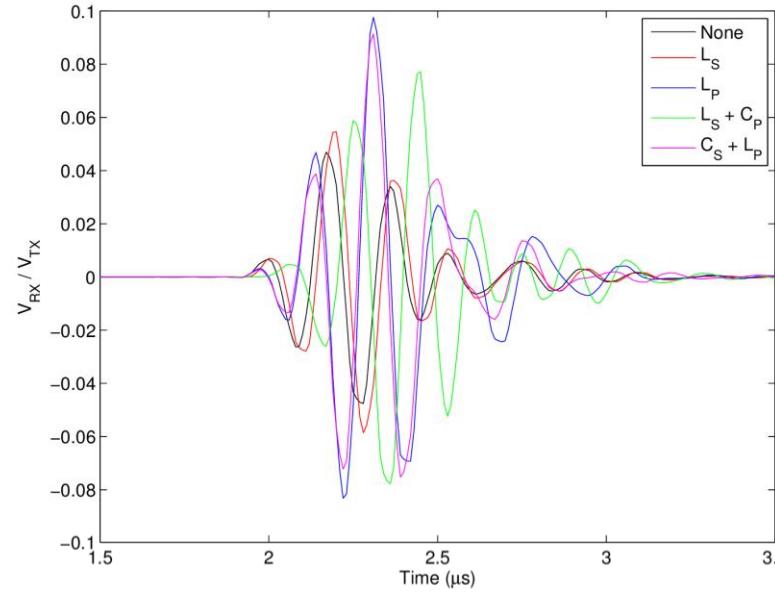Effect of matching circuits on Pulse Echo response




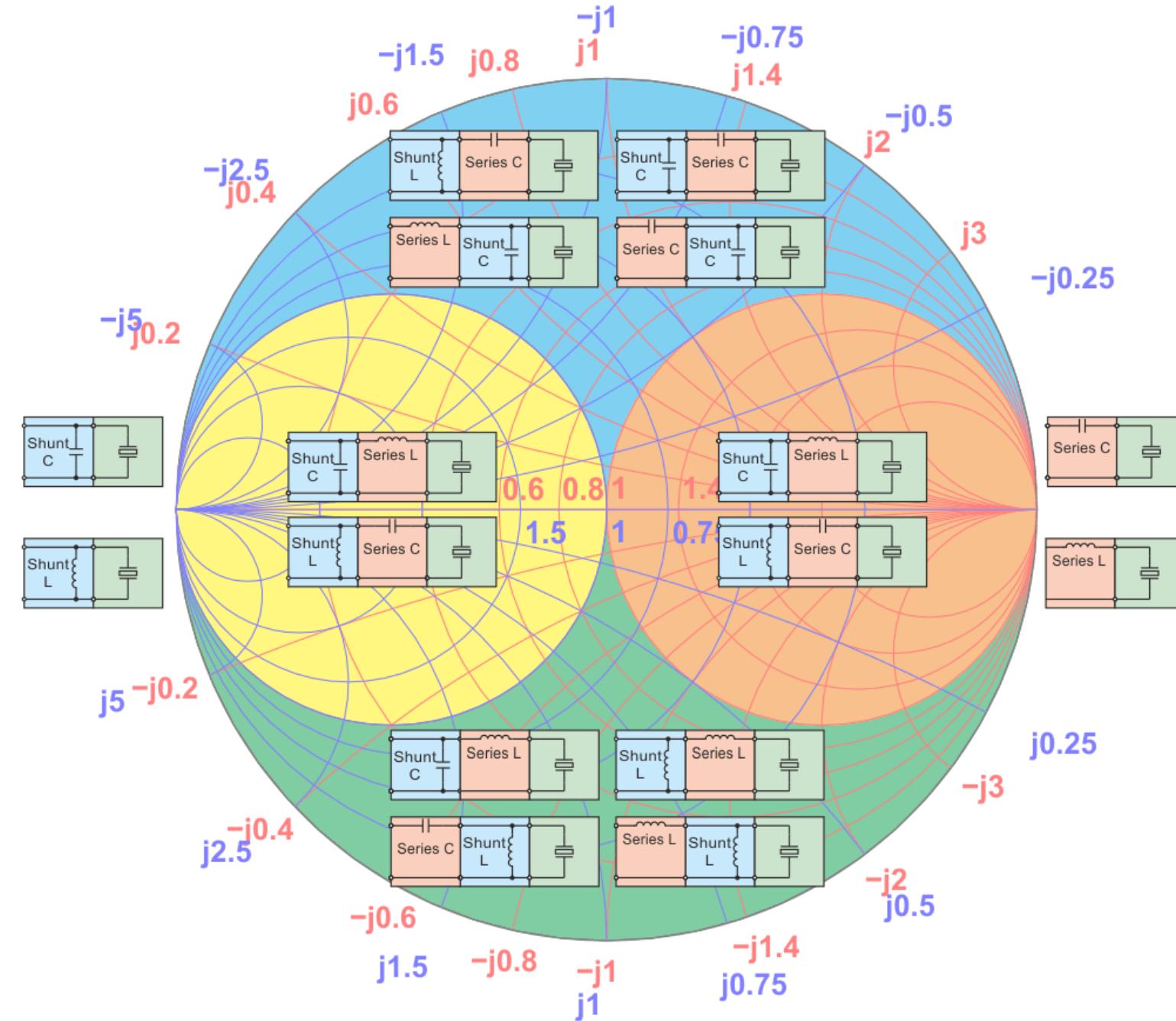- **Pulse echo time response**
- Improvement in sensitivity
 - $9.4 \text{ mV}_{RX}/\text{V}_{TX}$ (No matching)
 - $18.2 \text{ mV}_{RX}/\text{V}_{TX}$ (Parallel Inductor)
- **Pulse echo frequency response**
- Improved -6dB bandwidth
 - 2.5 MHz (No matching)
 - 3.5 MHz (Parallel Inductor)
 - Flatter bandwidth above -6dB




Electronics Overview

Transducer

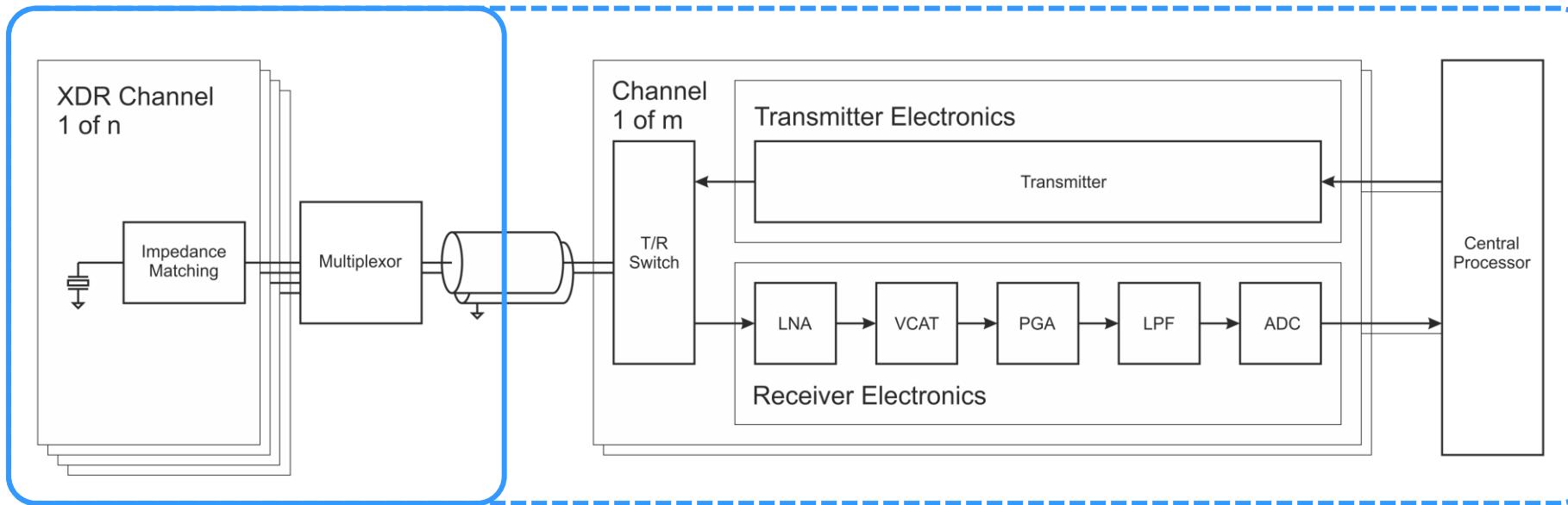

Arbitrary Excitation

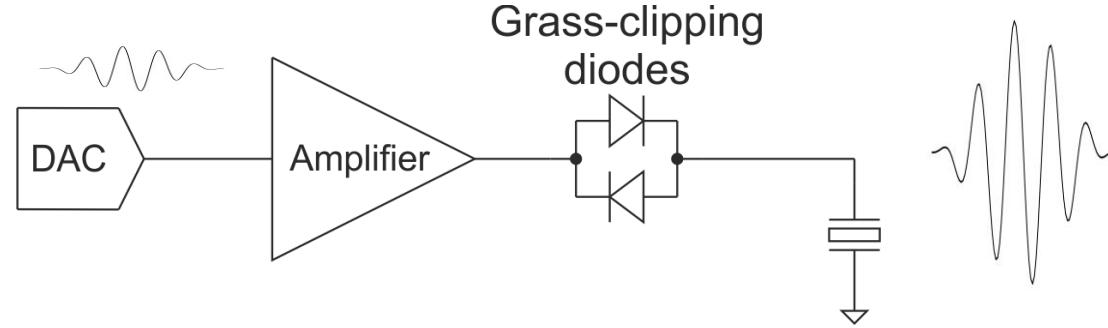

- True arbitrary excitation allows control of frequency/phase and amplitude.
- Arbitrary control required for apodization across an array aperture.
- Significant implementation complexity of digital to analog converter (DAC) and amplifier, plus digital control and waveform storage/generation requirements.
- Amplifier requires a linear, high current, high voltage, high slew rate response.
- Amplifier Slew rate (SR) defines frequency-voltage operating space:


$$2 \pi f V_{\text{pk}} \leq \text{SR} \leq \max \left(\left| \frac{d v_{\text{out}}(t)}{dt} \right| \right)$$
- Low output impedance of amplifier must be disconnected from transducer during receive mode using either a high voltage switch or grass-clipping diodes.



Pulsed & Switched Excitation


UNIVERSITY OF LEEDS

- Switching between discrete voltage levels to generate short pulses or ‘square wave’ signals.
- Potential for high voltages and currents to be switched at high freq.
- With decreasing rise and fall time signal approaches an impulse.
- Broadband pulse generation is limited by switching speed of MOSFET.
 - Performance limited by device parasitics
 - e.g. gate inductance, drain-source capacitance etc
- In negative ‘Shock Excitation’ the positive plate of charged capacitor switch to ground producing a negative pulse on transducer (top)
- Complex excitation modulation schemes (e.g. approximate to arbitrary excitation) can be implemented by direct switching between discrete supply voltages using multiple MOSFETs (bottom).

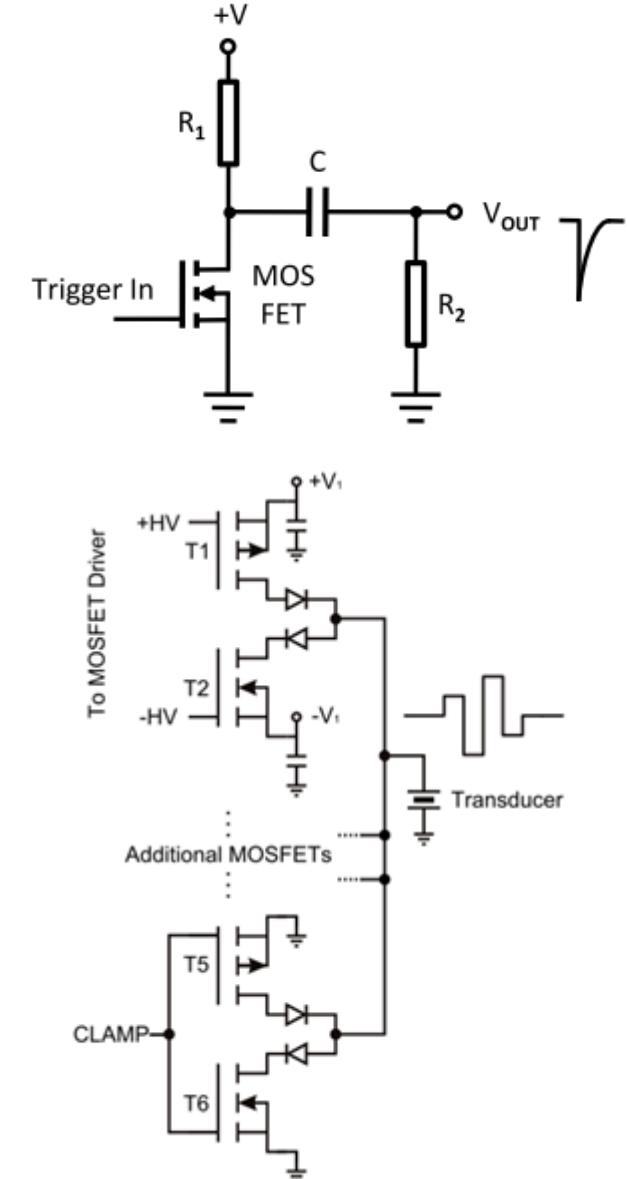


Commercial Chipsets

TX & T/R – Maxim – MAX14808

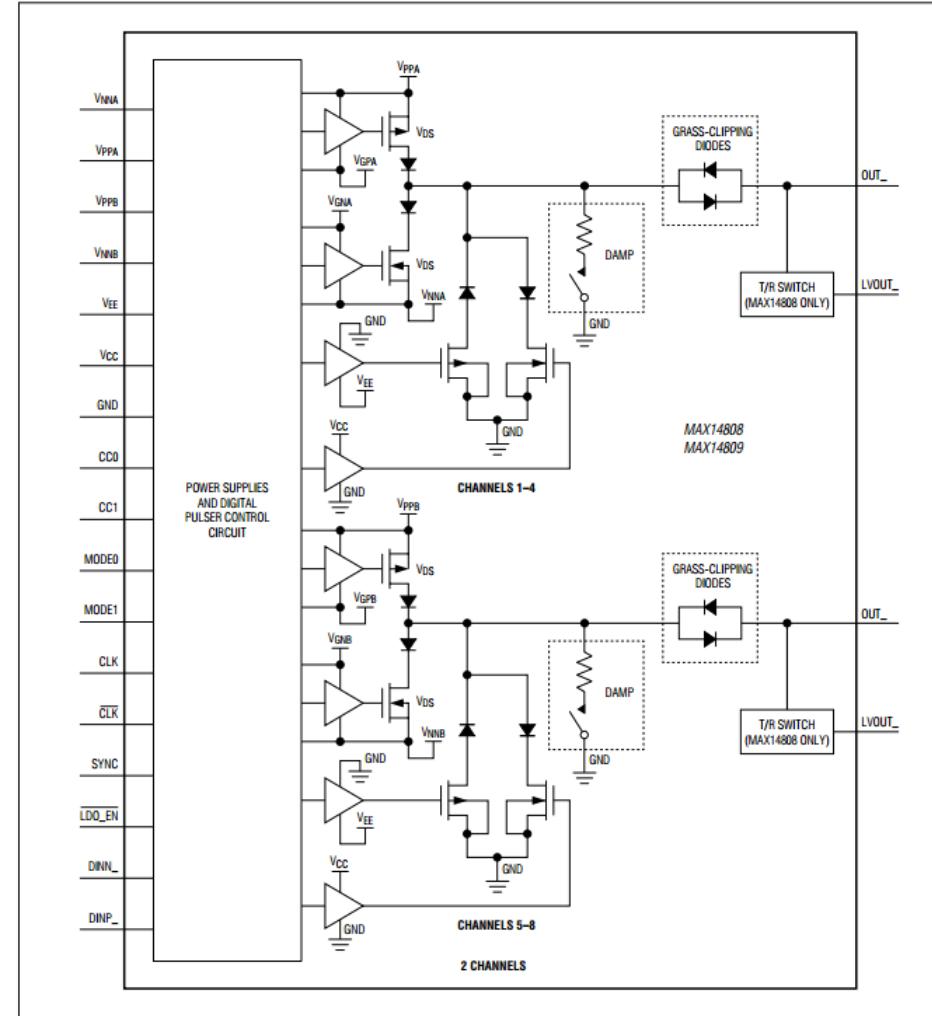


Transmit/Receive Switch

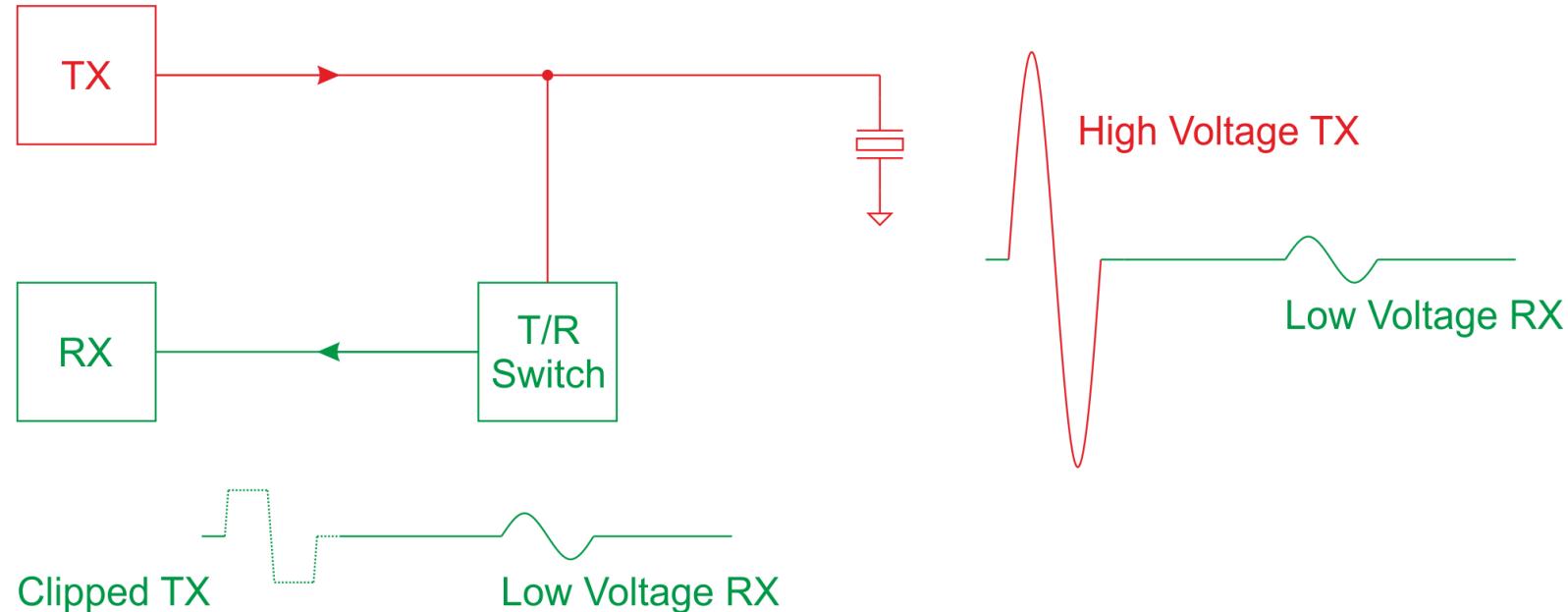- RX electronics are typically tolerant of input voltages in the order of ± 1 V.
- High voltages in the order of ± 100 V are common in excitation waveforms.
- Transmit/Receive (T/R) Switches are used to protect RX electronics from high TX voltages whilst allowing low voltage signals to RX electronics.
- T/R switch must be designed to minimise distortion to the RX signals.




Transmit/Receive Switch

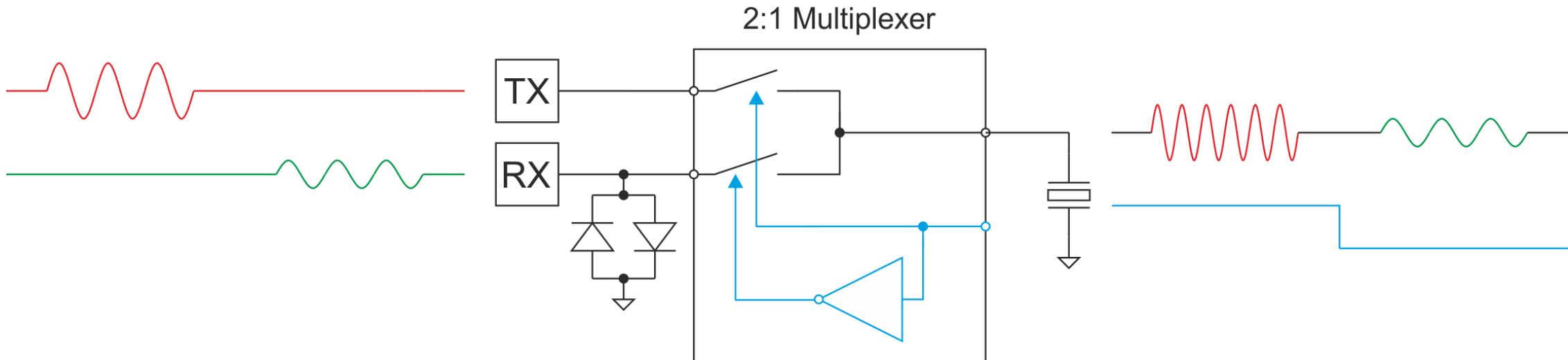- A multiplexer switch may be used as a T/R switch due to its inherent high voltage and low distortion.
- The switchover time between inputs must be very fast, ideally sub microsecond.
- Additional protection placed between T/R switch and receiver to protect sensitive electronics from high voltages that may present on transducer during switchover. Typically, back-to-back *grass clipping* diodes.




Diode Bridge T/R Switch

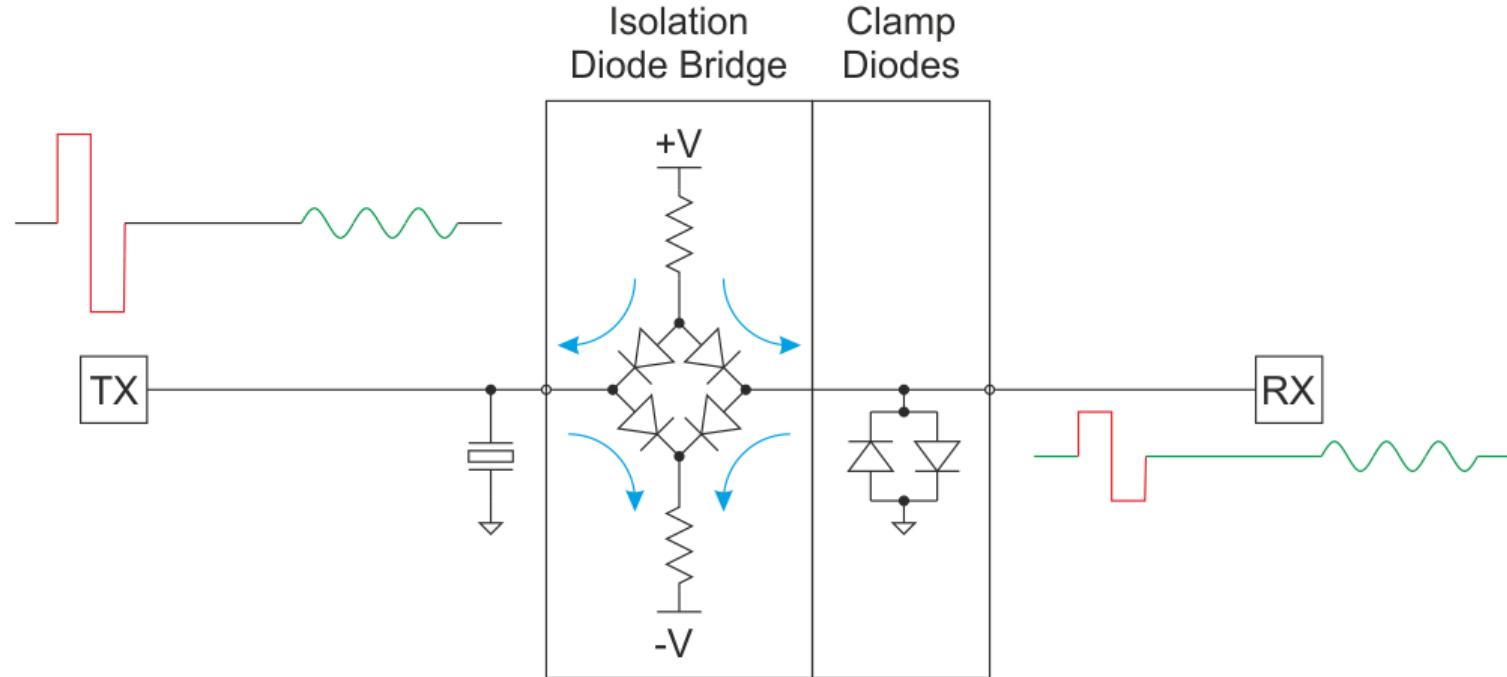- Diode bridge provides isolation of input and output voltages.
- Passive clamping of output voltage during transmit (or when high voltages present).
- Output mirrors input voltage during receive (or when low voltages present).
- Glass clipping clamping diodes provide further protection of output voltage.




Diode Bridge T/R Switch: RX

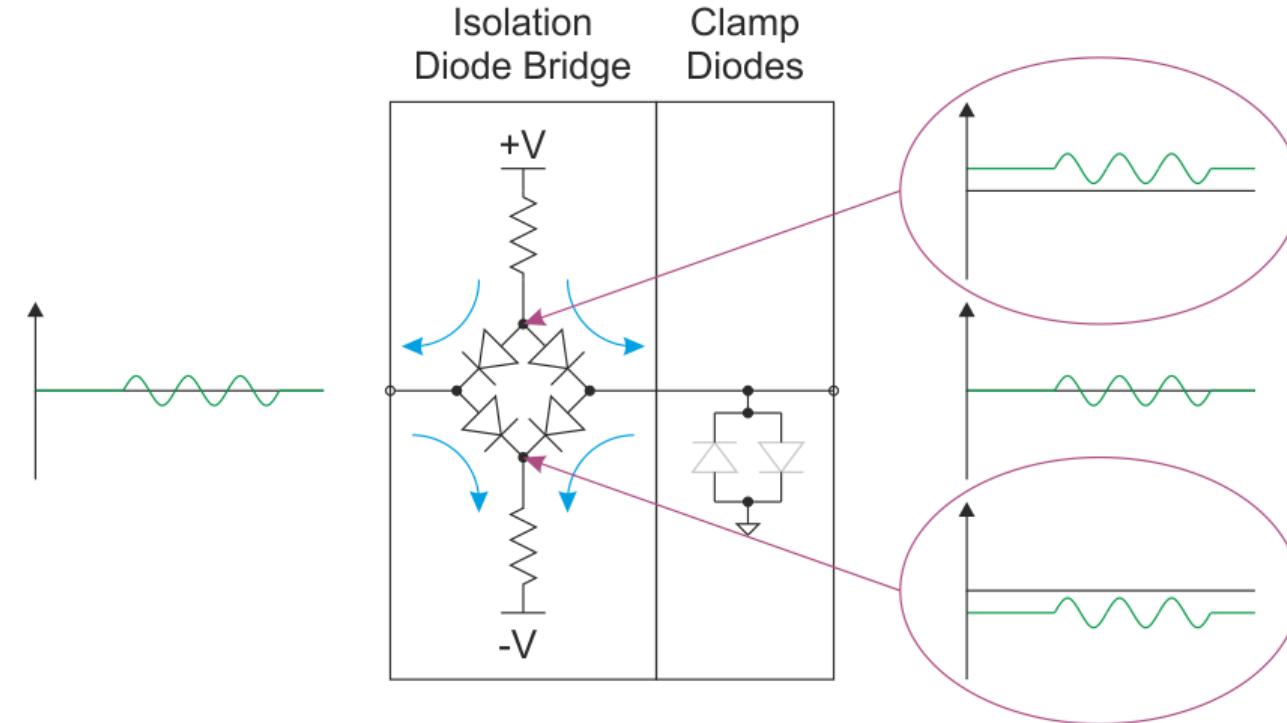- All isolation bridge diodes are forward biased.
- Clamp diodes are less than forward voltage – nominally non-conducting.
- Output voltage mirrors input voltage.




Diode Bridge T/R Switch: +TX

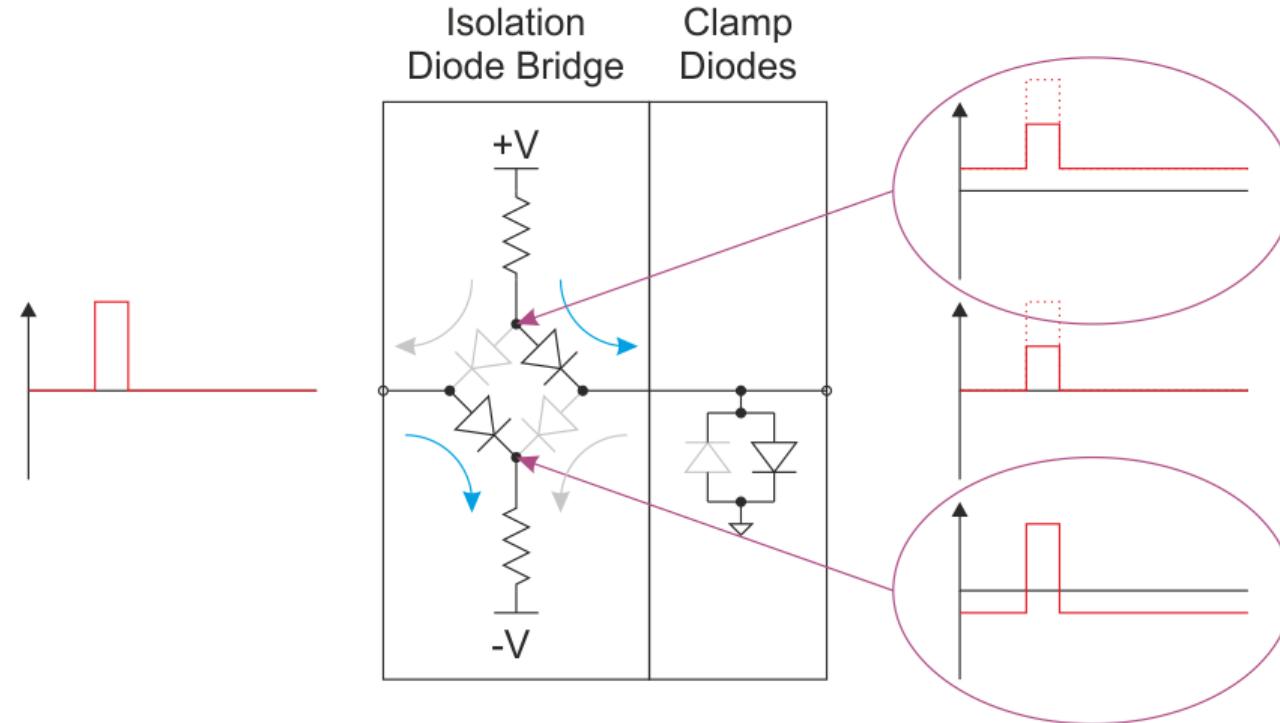- Input voltage high enough to reverse bias bridge diodes.
- Positive supply drives output positive.
- Clamp diodes restrict output voltage to safe level.



Diode Bridge T/R Switch: -TX

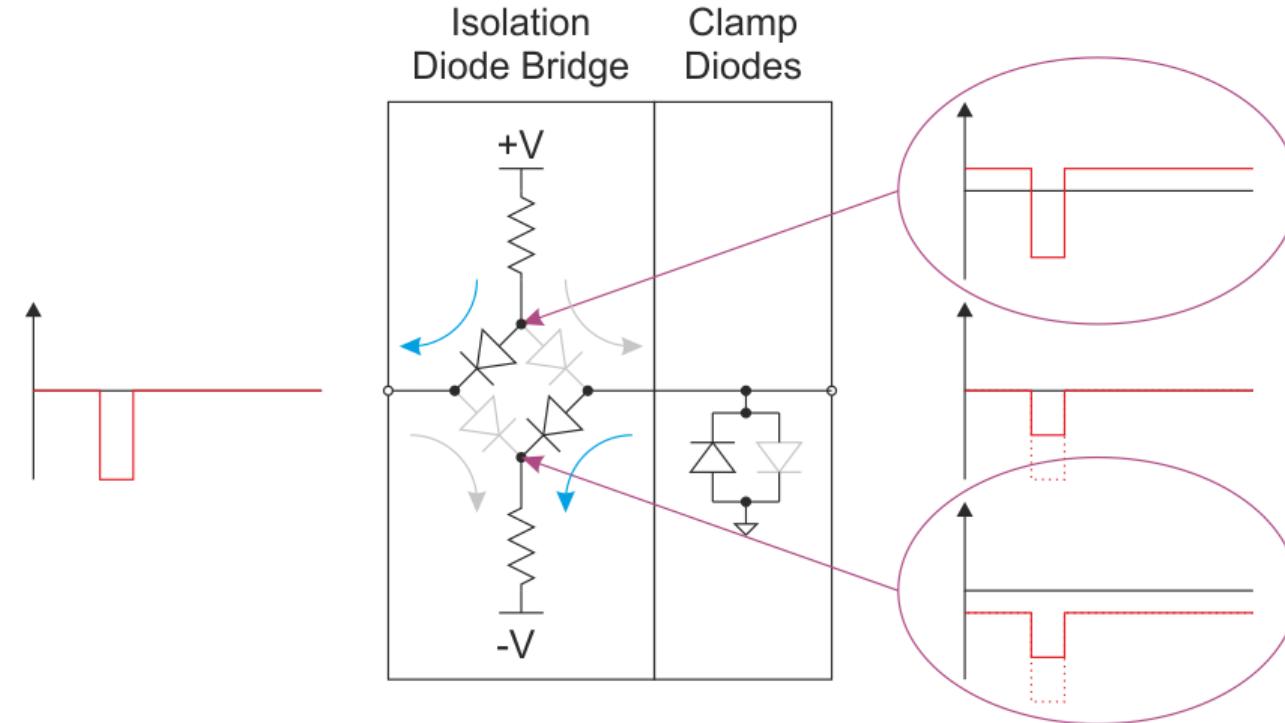- Input voltage low enough to reverse bias bridge diodes.
- Negative supply drives output negative.
- Clamp diodes restrict output voltage to safe level.



Commercial Chipsets T/R – Maxim – MAX9636


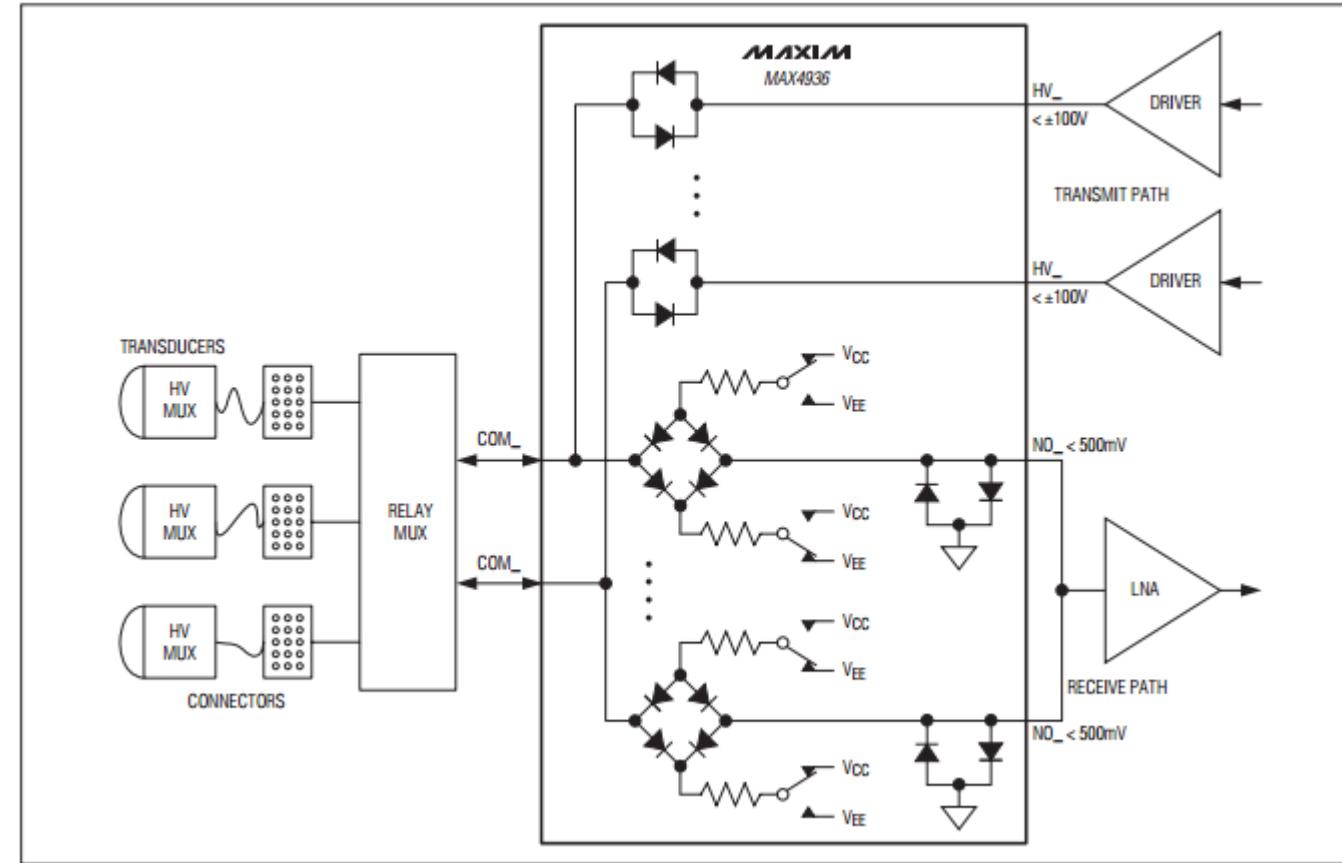


Image copyright Maxim Integrated (Source: MAX4936 Datasheet)


Multiplexers

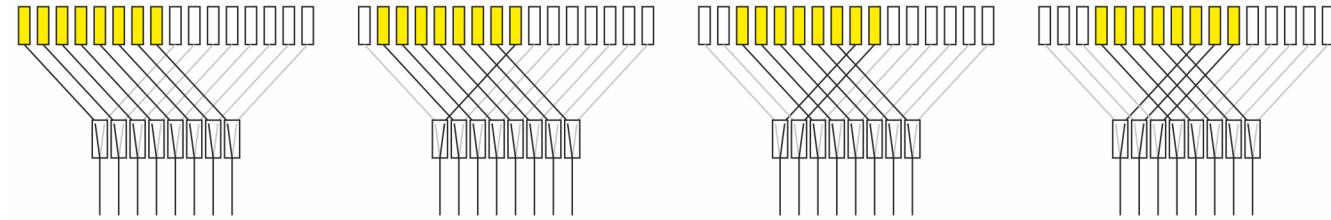- Example 256 element commercial linear probe.
- Multiplex [1 128], [2 129]... [127 255], [128 256]
- Any single aperture up to 128 consecutive channels.




- Within mapping limitations it is also possible to create:

Multiple apertures

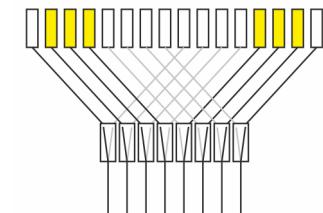

Sparse arrays

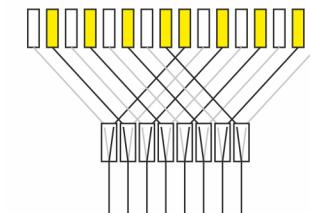


Time domain multiplexers

- Allow transducer elements to connect to a reduced number of TX/RX channels/cables
- Time domain switching of active elements between measurements.


Switching frequency < Pulse Repetition Frequency

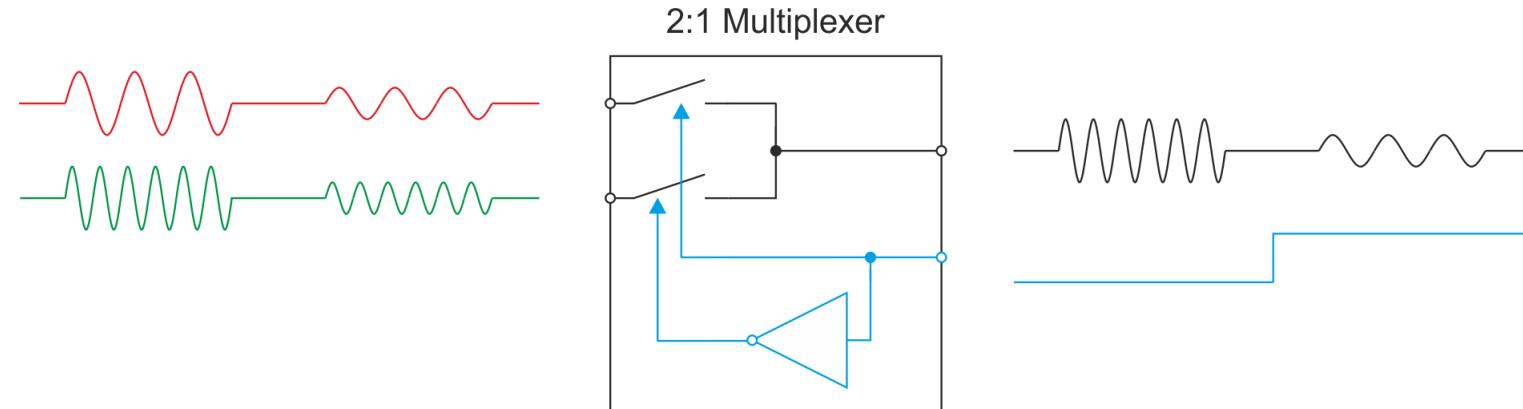- Limits techniques like full matrix capture as only a subset of elements can be concurrently addressed.
- A multiplexer switch must exhibit high voltage tolerance, high bandwidth, low distortion and low jitter characteristics.




HF time domain multiplexer

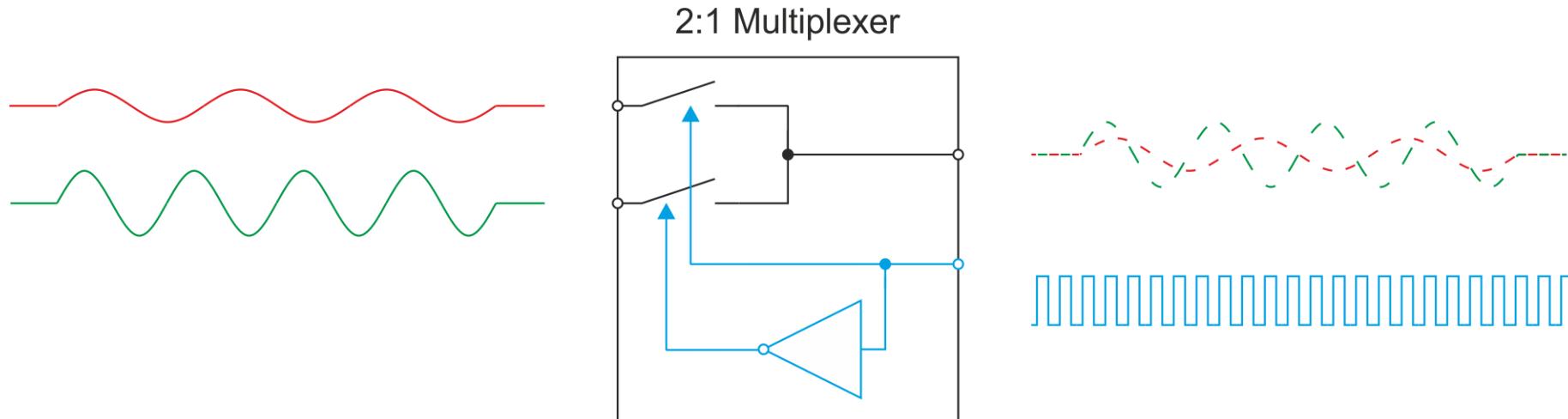- High frequency time domain modulation.
- Concurrent sampling of multiple signals.
- Increased signal bandwidth down a single coax cable.
- Requires high speed analog to digital converter in receiver.
- ‘Moving the ADC sample and hold buffer into the handle’.




Frequency domain multiplexer

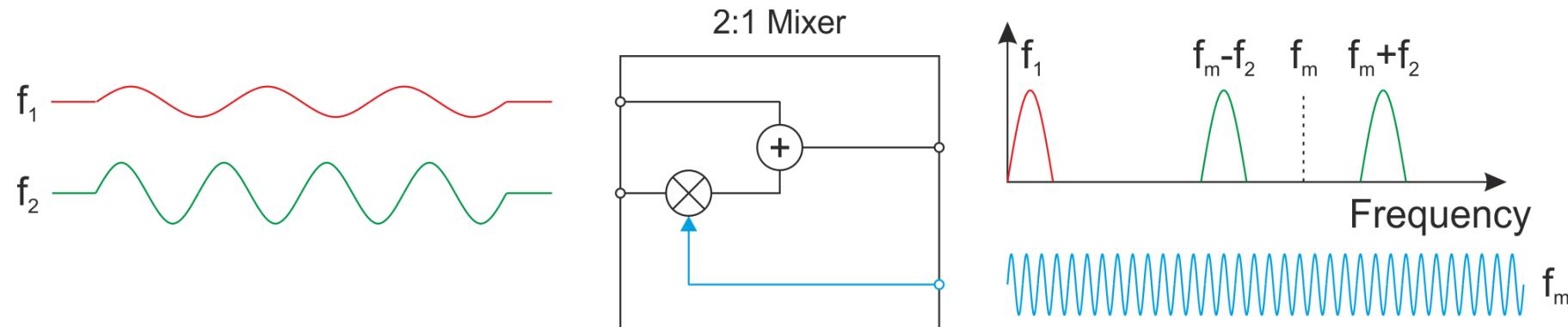- Frequency modulation of incoming signals to higher frequency.
- Increased signal bandwidth down a single coax cable.
- Requires high speed analog to digital converter in receiver.
- Requires **complex** demodulation in receiver.



Analog Front End (AFE)

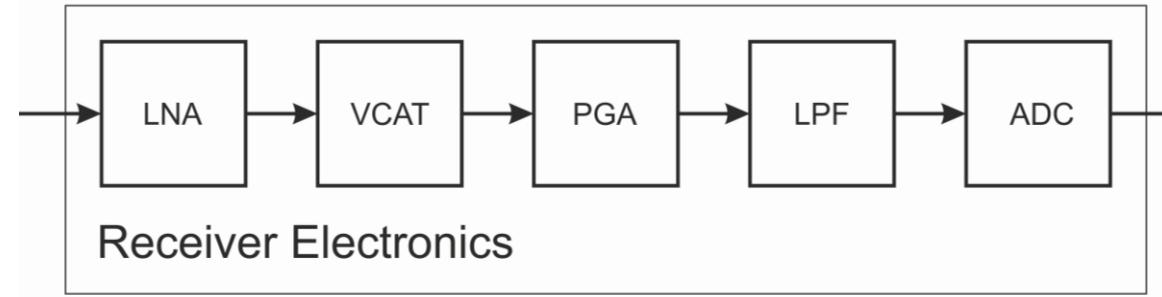


- **LNA** **Low Noise Amplifier**
- **VCAT** **Voltage Controlled Attenuator** (Time Gain Compensation)
- **PGA** **Programmable Gain Amplifier**
- **LPF** **Low Pass Filter** (Anti-aliasing filter)
- **ADC** **Analog to Digital Converter**

Commercial AFE Chipsets

Texas Instruments - AFE5807

UNIVERSITY OF LEEDS



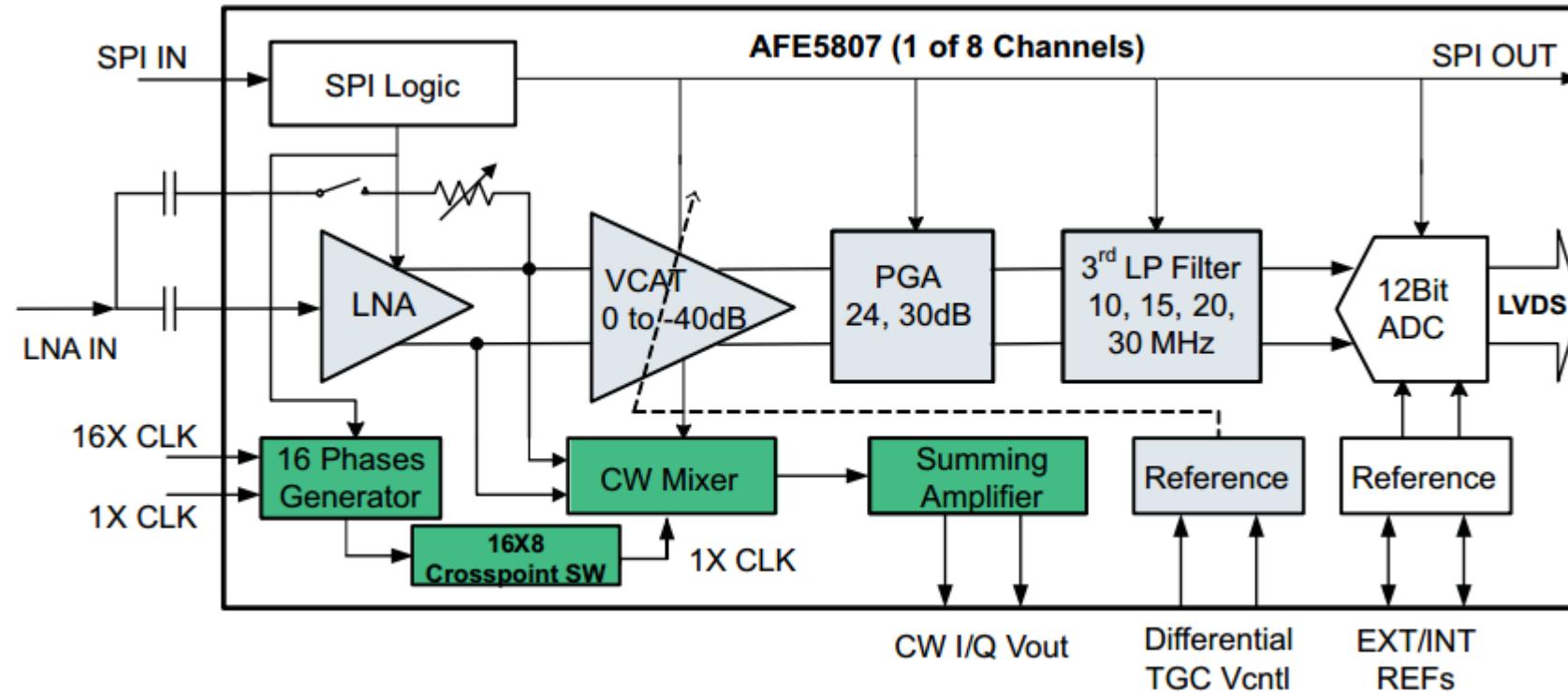


Sampling Theory

- Nyquist frequency f_n
- Sampling frequency f_s


$$f_n = \frac{f_s}{2}$$

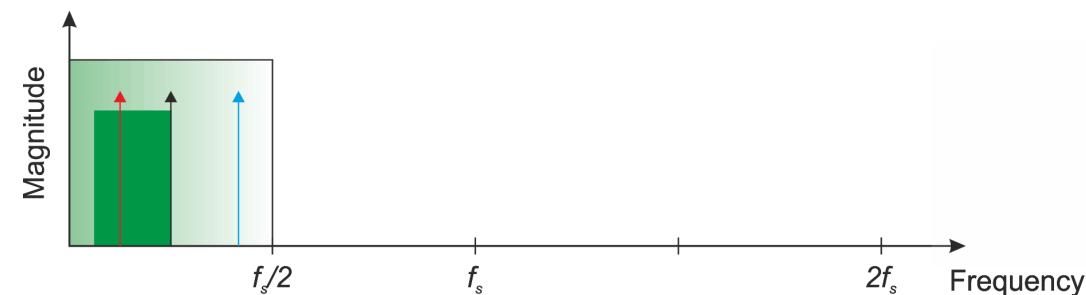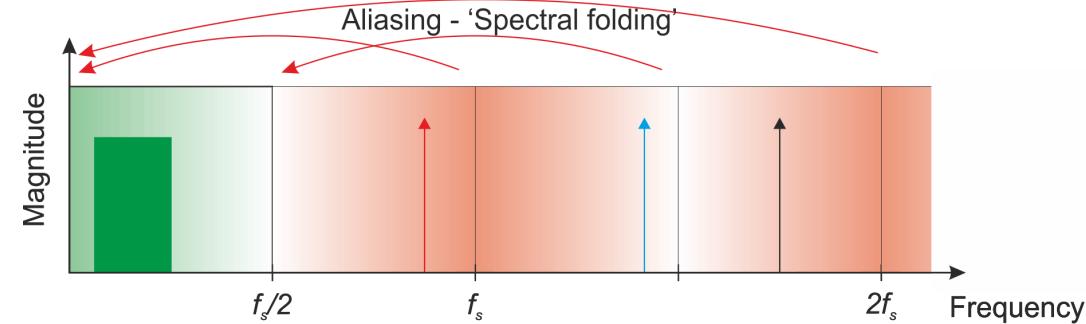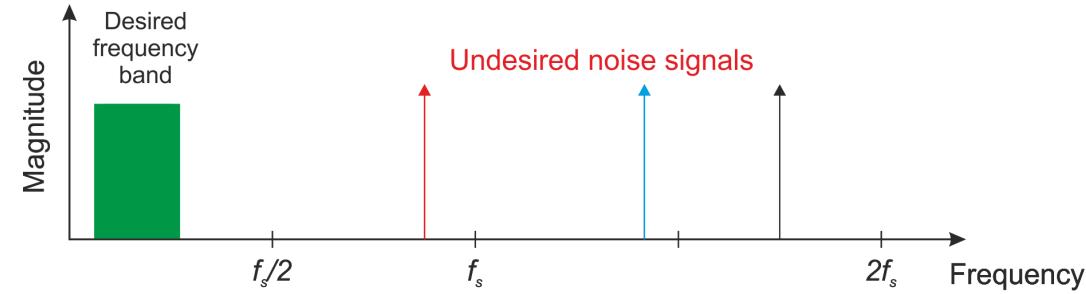- Beyond f_n frequencies alias of fold into the region zero to f_n .
- Digital filtering cannot be used to remove aliased frequencies.





Anti-aliasing filter

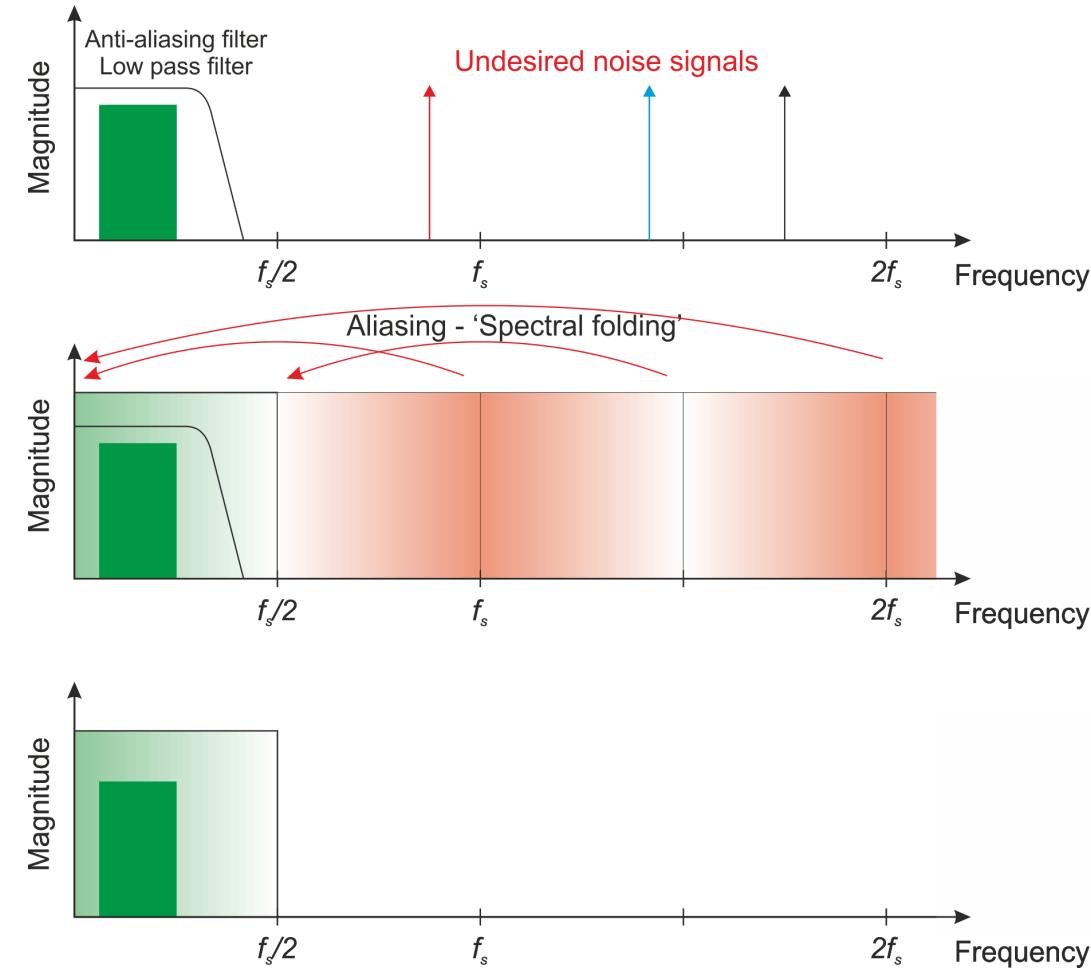- Prevention of aliasing requires analog filtering to be performed before the input to the ADC.
- The filter should be designed such that undesired frequencies are sufficiently suppressed before sampling.
- Sampling where the frequencies of interest are below the Nyquist frequency is termed oversampling
- Give consideration to parasitics when designing analog filters.




Passive Filtering

Low Pass, High Pass

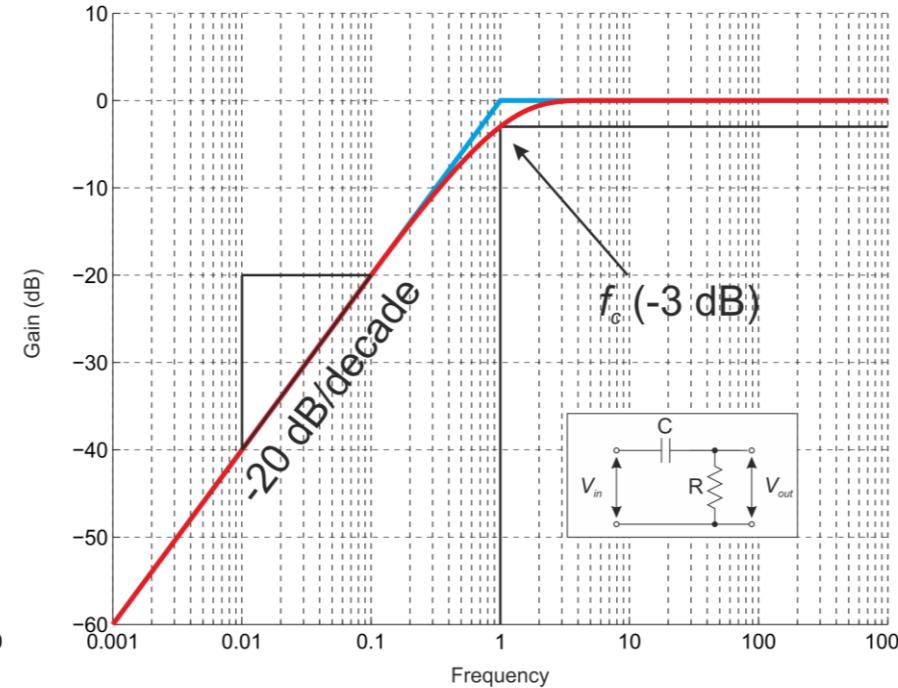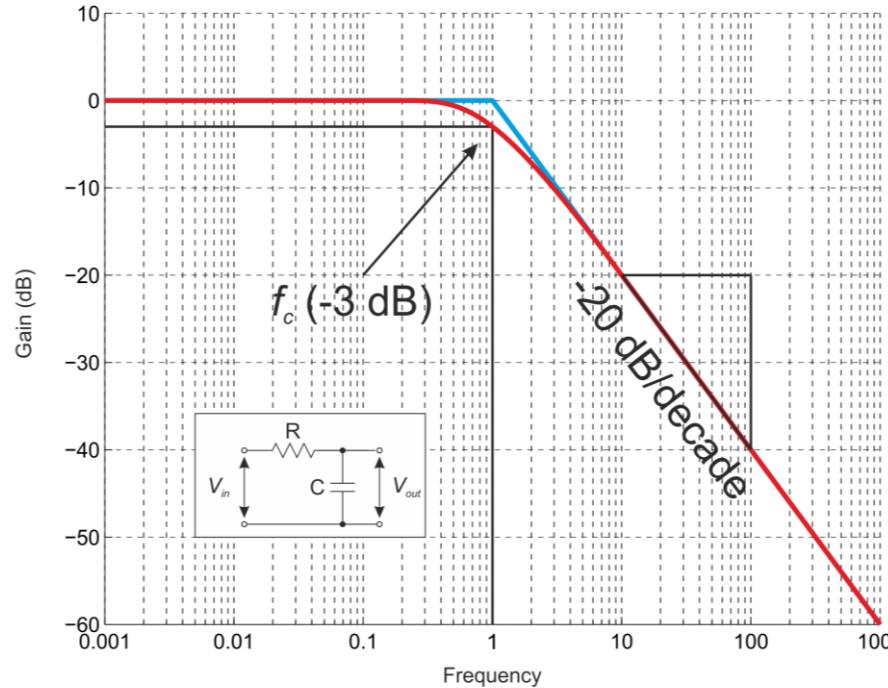

- The cut-off frequency, $f_c = \frac{1}{2\pi RC}$, defines the point of -3dB gain.
- Beyond the -3dB point, attenuation of -20 dB per decade frequency (roll-off)
- Cascade multiple stages for increased roll-off or bandpass and bandstop responses.
- Be aware of parasitic in lumped components – especially at high frequencies.

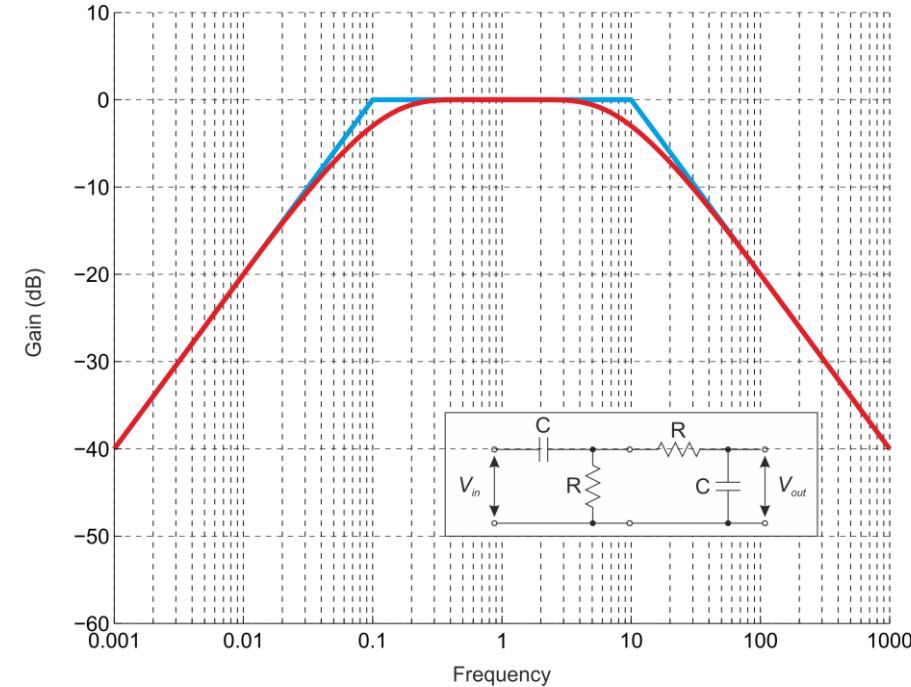
Analog Passive Filtering Cascaded Band Pass



- Multiple filter stages can be cascaded to form more complex filters.
- A band pass filters can be constructed by combining a low and high pass filter.
- Multiple cascaded low or high pass filters may result in a steeper roll-off.
- Beware of loading effects due to impedance of passive filters in series.
- Amplifier buffers may be required between stages to maintain desired impedance characteristics.

Active Filtering


3rd Order Low Pass

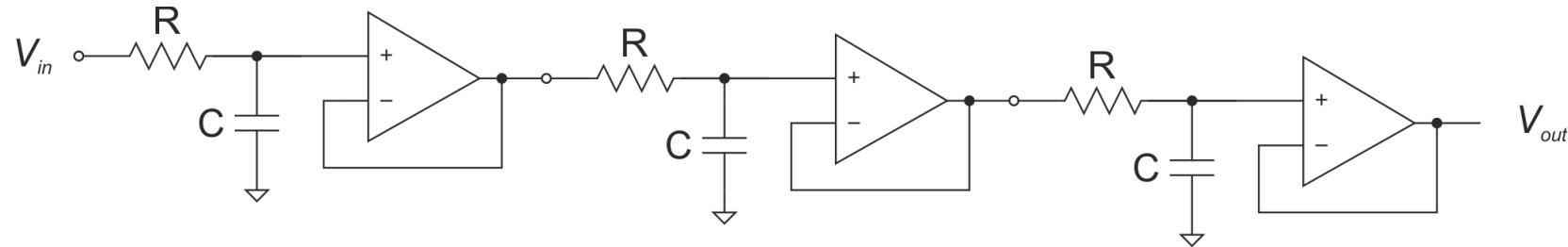


- Op-amps configured as unity gain buffers
- Are voltage followers: $V_{out} = V_{in}$
- High input impedance at the non-inverting input (+)
- Low output impedance to drive successive filter stages
- Input impedance is that of first the first stage RC filter

Time Gain Compensation (TGC) Voltage Controlled Attenuator (VCA)

- Typically implemented as a combination of fixed gain amplifier and time varying attenuation
- Voltage Controlled Attenuator (VGA) created using a voltage divider.
- Resistance between drain and source terminals of a Field Effect Transistor (R_{att}) can be controlled by varying gate voltage - Voltage Controlled Resistor (VCR)
- Control signal manipulated to produce controlled voltage-attenuation profile.
- Digital to analog converter used to control VGA and perform TGC.

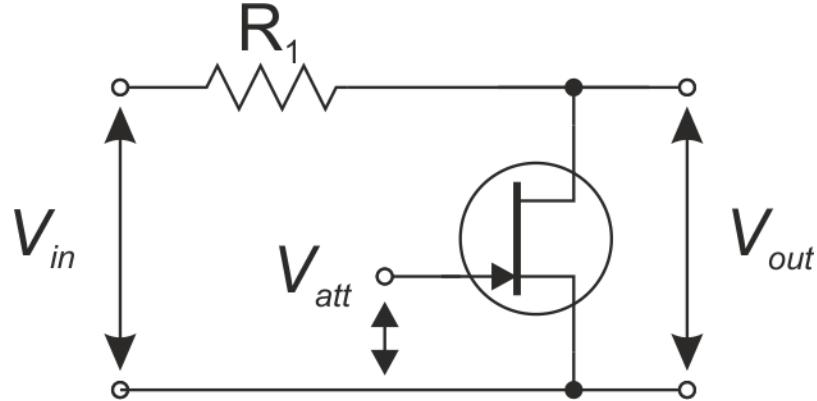
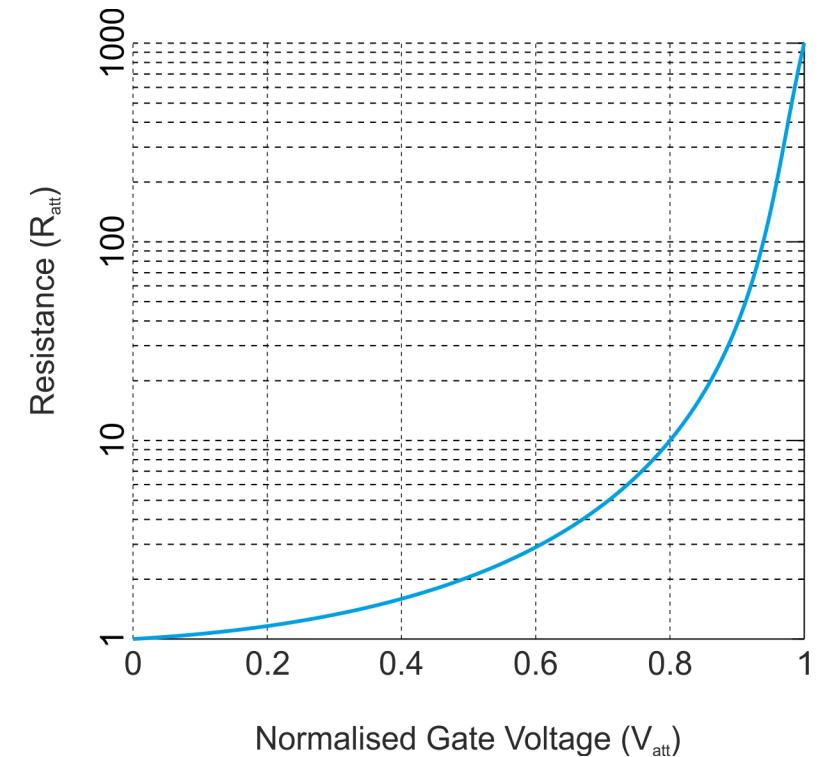
$$V_{out} = V_{in} \frac{R_{att}}{R_1 + R_{att}}$$



Simplified ADC Input

Sample


Charge input capacitor via input resistor
and wait for voltage to stabilise

Hold

Disconnect input resistor

Convert

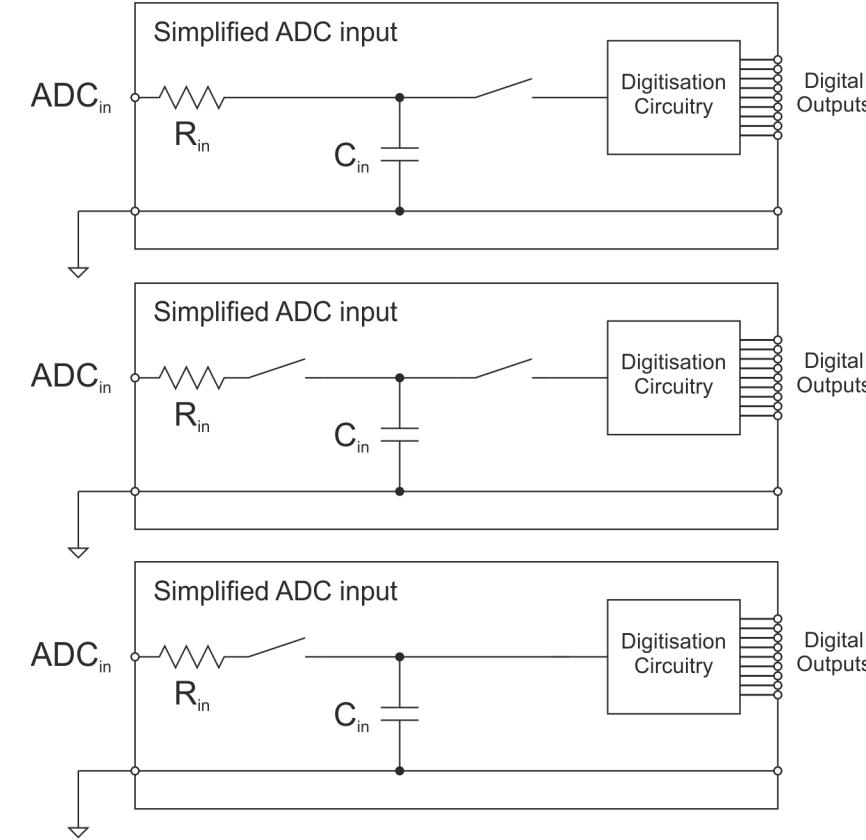Connect input capacitor to digitisation circuitry



- **Input resistor typically kilohms ($k\Omega$), Input capacitor typically picofarads (pF).**
- **Input typically acts as a low pass filter with very high cut off frequency.**
- **Input not matched to characteristic impedance - Buffering or matching required!**

Sampling theory

Ideal Signal to Noise Ratio

$$SNR = 6.02n + 1.76$$


where n is the number of bits

n (bits)	Ideal SNR (dB)
8	49.92
10	61.96
12	74.00
14	86.04
16	98.08

- SNR should be greater than the desired dynamic range of the imaging system.
- **Ideal SNR can never be achieved in a practical system**

Sampling clock jitter and SNR

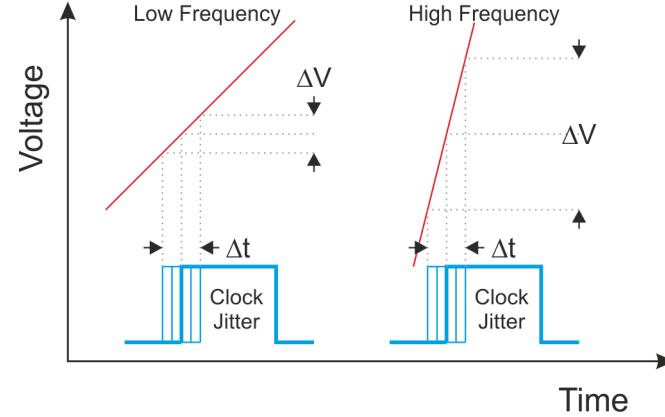
- SNR should be greater than the desired dynamic range of the system.
- Ideal SNR can never be achieved in a practical system.
- Clock jitter is a time deviation for the ideal period clock crossing point



$$\text{SNR} = -20 \log_{10}(2\pi f_{in} t_j)$$

f_{in} Input frequency (Hz)


t_j Sampling Clock Jitter (s)

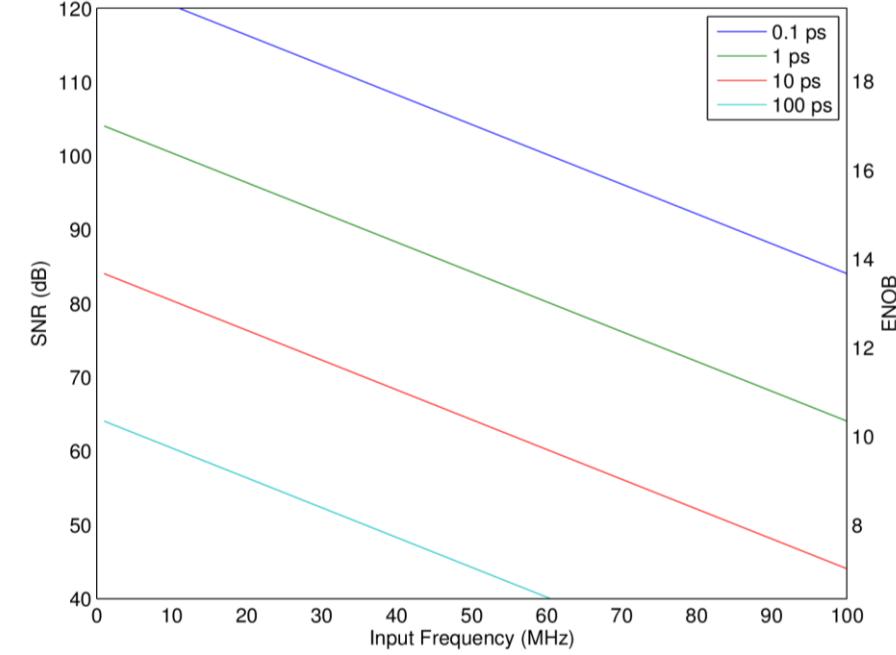

e.g. 50 MHz input to 12 bit ADC requires clock jitter <1 ps – 16 bit requires 100 fs!

Jitter is not dependent on sampling frequency!

Differential signalling

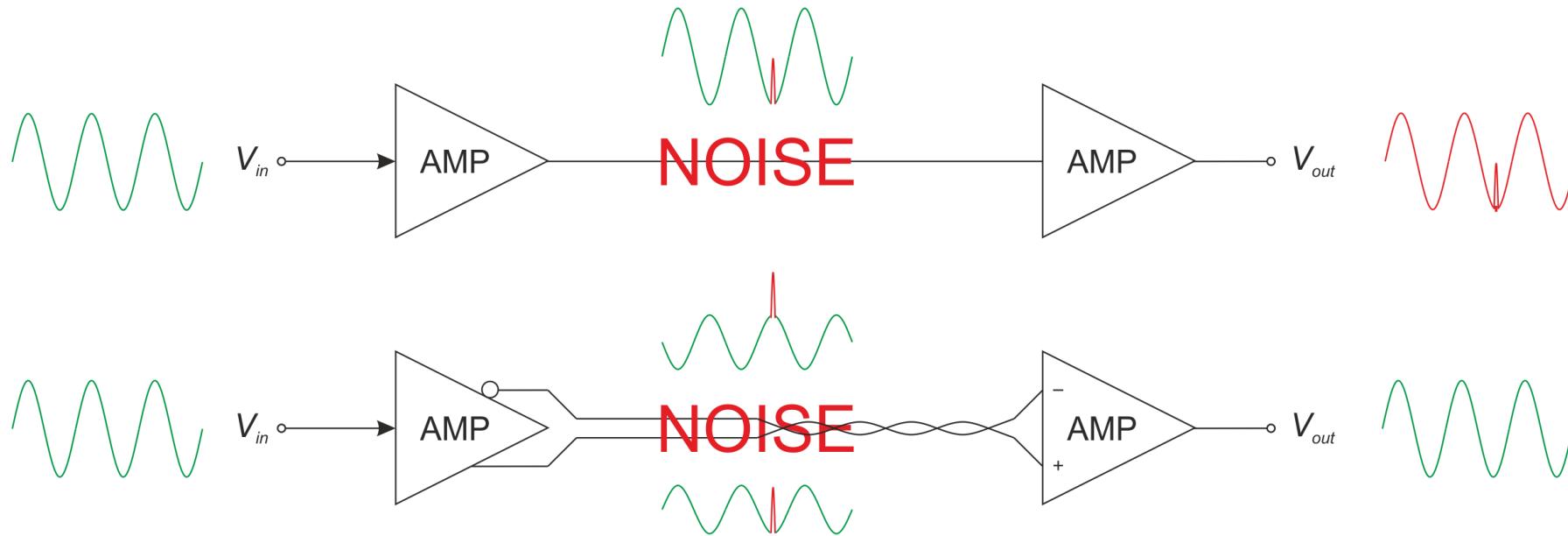

- Differential signalling reduces noise in transmission of signals in electrically noisy environments.
- A signal is transmitted along with its inverse signal through a close couple path (IC, PCB trace, twisted pair cable) where signals on both paths are subjected to equal additive noise.
- Original signal is recovered at receiver by subtracting the negative signal from the positive signal.
- $\text{Signal} - \text{negative Signal} = 2 \times \text{Signal.}$ $\text{Noise} - \text{Noise} = 0$

Thank you!

